

BIPOLAR JUNCTION TRANSISTOR (BJT)

* A semi-conductor device that can amplify electronic signals as radio and television signals

→ Advantages of transistor:

i) low operating voltage

ii) Highest efficiency.

iii) Small size & ruggedness.

iv) Does not require any filament power.

Olden days

Vacuum tubes.

→ Transistor is a 3 terminal device:

i) Base

ii) Emitter

iii) Collector

* According to config., it can be used for voltage or current amplification.

→ It can be operated in 3 config.

* Common emitter

* Common base

* Common collector.

* The input signal of small amplitude is applied at the base to get the magnified output signal at collector.

→ Two types of transistor:


* Unipolar juncⁿ transistor (UJT)

↳ Current conduction is only due to one type of carriers

* Bipolar juncⁿ transistor [BJT]

↳ Conduction due to both holes & e^- .


* The amplification in the transistor is achieved by passing input current signal from a region of low resistance to high resistance

→ Two types of BJT —  NPN Type
PNP Type

→ BIASED TRANSISTOR :

The transistor works in one of the three regions :

Region	E-B Junc ⁿ	C-B Junc ⁿ
Active	Forward	Reverse
Cut-off	Reverse	Reverse
Saturation	Forward	Forward

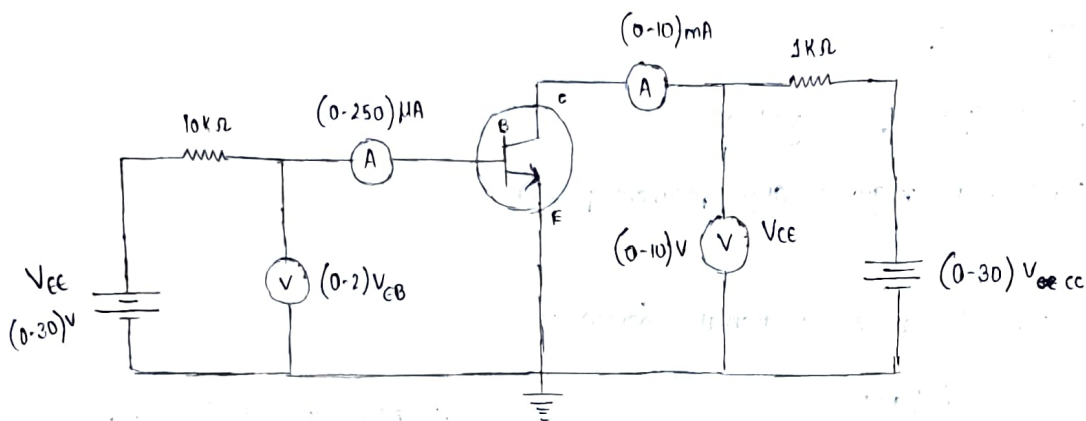


$V_{BE} \rightarrow \text{const.}$, $V_{CE} \rightarrow \text{const}$

$V_{CE} \rightarrow \text{varied}$ & corresponding readings of base current are noted $[I_B]$.

$I_B \rightarrow \text{const}$

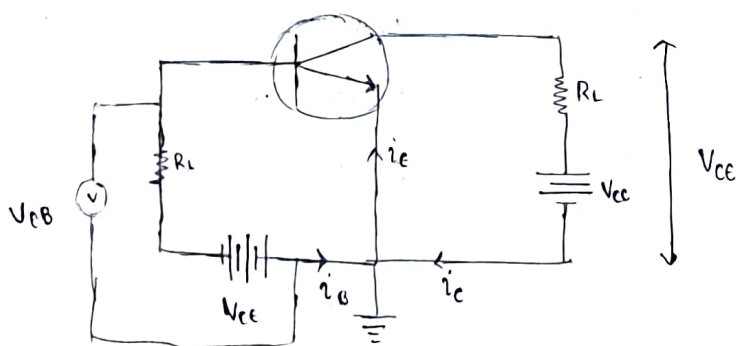$V_{CE} \rightarrow \text{varied}$ & corresponding readings of collector current are noted (I_C) .





OPERATIONAL AMPLIFIER [OP AMP]

* An operational amplifier is a direct coupled, high gain, amplifier with feedback. It is commonly known as 'opamp'.

This is called so because of its ability to perform mathematical operations such as addition, int., diff., etc.

→ Block diag. of opamp:

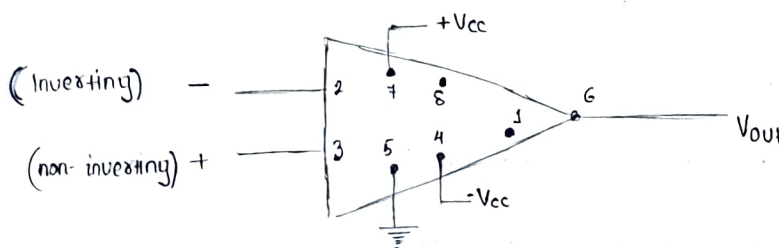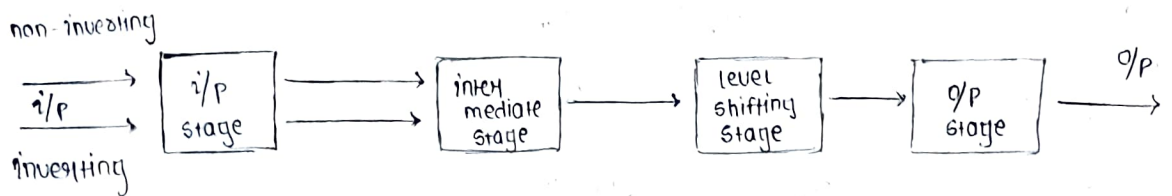

opamp
in
diagram

* Input stage:

It is a dual i/p, double ended o/p differential amplifier.

It has highest gain

* Intermediate stage:

It is a dual i/p, single ended o/p differential amplifier.

It also provides some amplification.

* Level shifting stage:

It is an emitter follower circuit. It shifts the o/p of intermediate stage to zero dc voltage w.r.t ground.

* Output stage :

It is a push pull complementary amplifier to raise the current supplying capacity, to increase o/p voltage ~~drift~~ swing and to provide low o/p resistance

→ Properties of an ideal opamp :

- * open loop voltage gain is infinity ($A_v = \infty$)
- * A large voltage gain when operating without feedback
- * Input impedance is infinity ($Z_{in} = \infty$)
- * o/p impedance is zero ($Z_{out} = 0$)
- * Bandwidth is infinity ($BW = \infty$)
- * Common mode rejection ratio is infinity ($CMRR = \infty$)
- * Slow rate is ∞
- * Perfect balance is $V_o = 0$, when $V_1 = V_2$
- * Characteristics do not vary with temperature
- * Voltage gain remains constant over a wide freq. range

→ Slow rate of opamp :

It is defined as the max rate of change of o/p voltage/~~unit~~ per unit of time. It is expressed in volts/microsecond.

$$SR = \left(\frac{dV_o}{dt} \right)_{\max} \text{ V}/\mu\text{sec.}$$

→ Open loop gain of opamp :

open loop gain (A_v) of an opamp is the ratio of o/p voltage (V_o) to the differential i/p voltage (V_{id}) without feed back.


$$A_v = \frac{V_o}{V_{id}}$$

→ CMRR of an opamp :

It is a measure of ability of opamp to suppress the common mode signals. It is defined as ratio of differential mode gain to the common mode gain

$$CMRR = \frac{\text{Diff. mode gain}}{\text{Common mode gain}} = \frac{A_d}{A_{cm}}$$

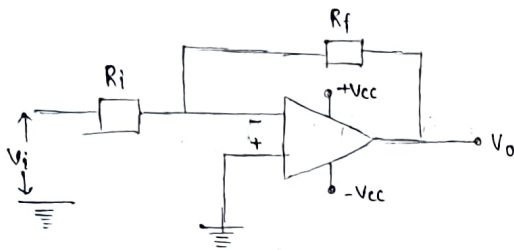→ Circuit diagram of an inverting amplifier and its o/p expression.




$$V_o = -\frac{R_f}{R_i} \cdot V_i$$

Gain of inverting amplifier :


$$\text{Gain } A_{v_f} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

where R_f = feed back resistance

R_i = i/p resistance

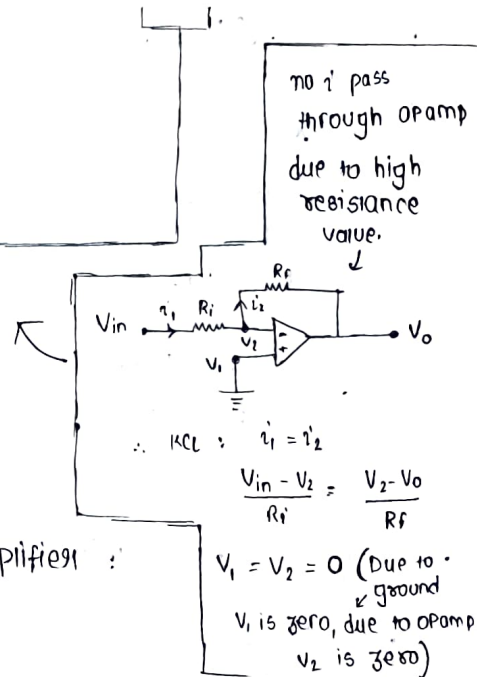

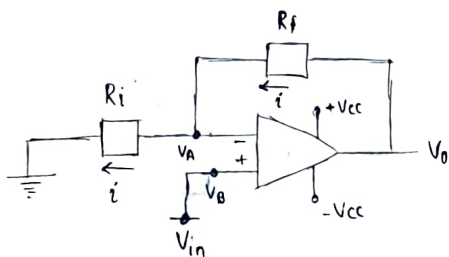→ Circuit diag. of a non-inverting amplifier :



$$V_o = \left(1 + \frac{R_f}{R_i}\right) \cdot V_i$$

$$\frac{V_o}{V_i} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

Gain expression : $A_{v_f} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$

$$V_{in} = V_A = V_B, \quad i = \frac{V_o - V_A}{R_f} = \frac{V_o - V_{in}}{R_f}$$

$$i = \frac{V_A - 0}{R_i}$$

$$i = i$$

$$\frac{V_o}{R_f} - \frac{V_{in}}{R_f} = \frac{V_{in}}{R_i} \Rightarrow \frac{V_o}{R_f} = V_{in} \left[\frac{1}{R_f} + \frac{R_f}{R_i} \right] \Rightarrow V_o = \left[1 + \frac{R_f}{R_i} \right] V_{in}$$

Investing

* Input voltage is applied to investing terminal of opamp through R_i

* Voltage shunt feedback is used

* The o/p is phase reversed.

* Gain : $A_{vf} = -\frac{R_f}{R_i}$

⇒ Draw the ckt diagram of non-inverting amplifier with a feedback gain of 30

Soln


$$A_{vf} = 30$$

$$1 + \frac{R_f}{R_i} = 30$$

$$R_f = 29 R_i$$

Assume, $R_i = 10 \text{ k}\Omega$

$$R_f = 290 \text{ k}\Omega$$

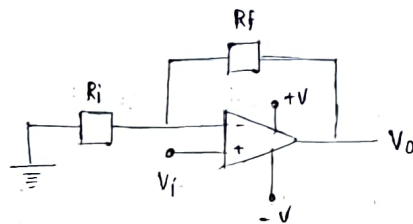

⇒ Design a ckt using opamp to get an o/p of 6V from an i/p of 2V

Soln

$$V_o = 6\text{V}, \quad V_i = 2\text{V}$$

$$R_f = ?$$

for non-inverting amplifier.

$$V_o = \left(1 + \frac{R_f}{R_i}\right) \cdot V_i$$

$$R_f = 2 R_i$$

Assume, $R_i = 10 \text{ k}\Omega$

$$R_f = 20 \text{ k}\Omega$$


Non-inverting

* Input voltage is directly applied to non-inverting terminal of opamp.


* Voltage series feedback is used

* The o/p is inphase with the i/p

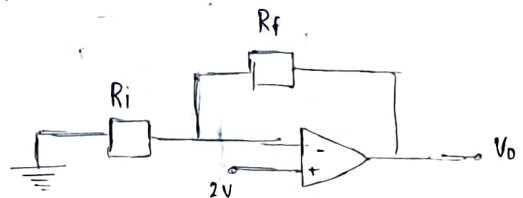* Gain : $A_{vf} = \left(1 + \frac{R_f}{R_i}\right)$



→ ADDER / SUMMER CKT using opamp :

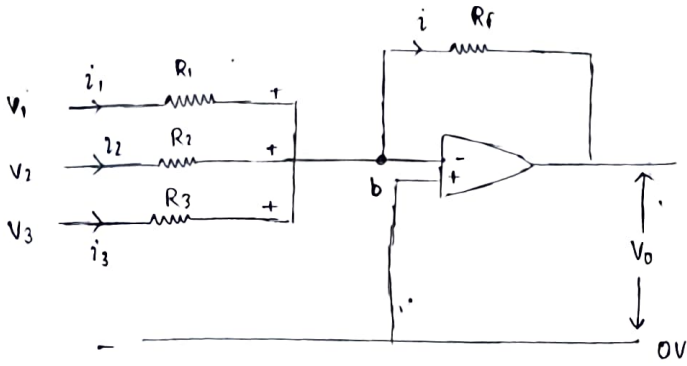

* Calculations :

$$i_1 = \frac{V_1}{R_1}, \quad i_2 = \frac{V_2}{R_2}, \quad i_3 = \frac{V_3}{R_3} \quad \& \quad i = -\frac{V_0}{R_f}$$

★ KCL at point 'b' :

$$i_1 + i_2 + i_3 = i$$

$$\Rightarrow -V_0 = R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$


$$\text{if } R_1 = R_2 = R_3 = R_f = R$$

$$\Rightarrow V_0 = -\frac{R_f}{R} [V_1 + V_2 + V_3]$$

$$\Rightarrow V_0 = -K [V_1 + V_2 + V_3]$$

→ Thus the voltages are added and amplified

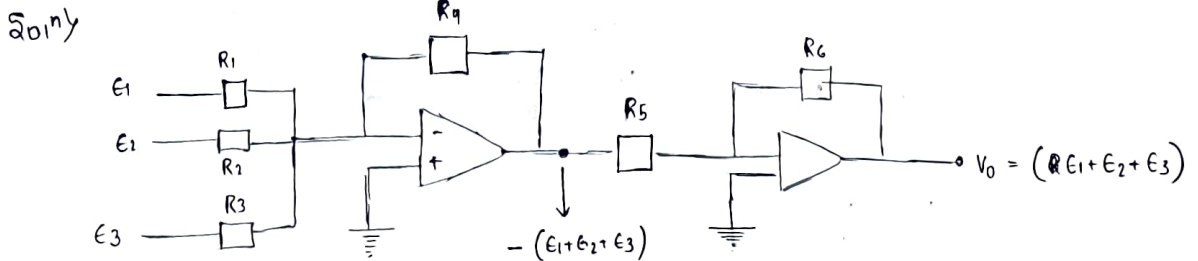
⇒ Draw ckt diag. using opamp to get o/p vol of $E_1 + E_2 + E_3$.



$$\text{Cond}^n : R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R$$

→ DIFFERENTIAL AMPLIFIER: [Deriving V_o eqⁿ in terms of i/p's]

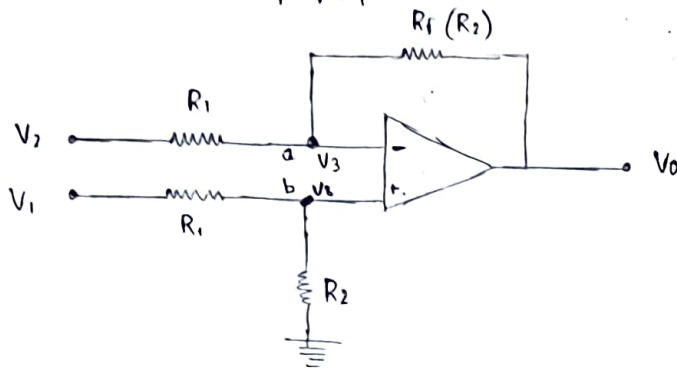A ckt that amplifies the diff b/w two signal is called difference or differential amplifier.



The eqⁿ at 'a' is : $\frac{V_3 - V_2}{R_1} + \frac{V_3 - V_o}{R_2} = 0 \rightarrow (1)$

The eqⁿ at 'b' : $\frac{V_3 - V_1}{R_1} + \frac{V_3}{R_2} = 0 \rightarrow (2)$

$(2) - (1) \Rightarrow V_o = \frac{R_2}{R_1} [V_1 - V_2]$

} Imp deviation.
↓ down

where $R_2 = R_f \rightarrow$ feedback resistor.

* Such a ckt is very useful in detecting very small difference in signals, since the gain R_2/R_1 can be chosen to be very large
for ex: If $R_2 = 100 R_1$, then a small diff. $(V_1 - V_2)$ is amplified 100 times.

$(1) \rightarrow \frac{V_3}{R_1} + \frac{V_3}{R_2} - \frac{V_2}{R_1} - \frac{V_o}{R_2} = 0$

$\Rightarrow V_3 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2}{R_1} = \frac{V_o}{R_2}$

$(2) \rightarrow \frac{V_3}{R_1} - \frac{V_1}{R_1} + \frac{V_3}{R_2} = 0$

$\Rightarrow V_3 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_1}{R_1}$

$\therefore (1) - (2) = -\frac{V_2}{R_1} = \frac{V_o}{R_2} - \frac{V_1}{R_1}$

$= \frac{1}{R_1} [V_1 - V_2] = \frac{V_o}{R_2} \Rightarrow V_o = \frac{R_2}{R_1} [V_1 - V_2]$

If R_1 is not same in V_2 & V_1 then use derivation to solve