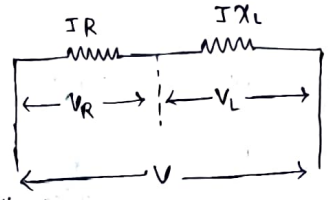


~~Page~~


RESISTANCE - INDUCTANCE (R-L) series circuit :

- * In series, same amount of i flows through all elements
so, current should be taken as reference.





- * $V_R = iR$, $V_L = iX_L$

- * In resistor :

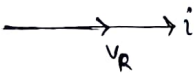

- In Inductor :

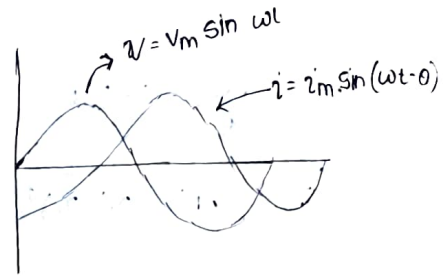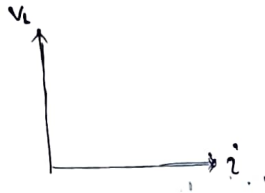

- * $V^2 = V_R^2 + V_L^2$

$$\Rightarrow V = \sqrt{V_R^2 + V_L^2} = \sqrt{(iR)^2 + (iX_L)^2} = \underline{\underline{I \sqrt{R^2 + X_L^2}}}$$

$$\Rightarrow i = \frac{V}{\sqrt{R^2 + X_L^2}} = \underline{\underline{\frac{V}{Z}}}$$

- * $\tan \theta = \frac{V_L}{V_R} = \underline{\underline{\frac{X_L}{R}}}$

- * $X_L = \omega L = 2\pi fL$

- * Power factor $\Rightarrow \cos \theta = \underline{\underline{\frac{R}{Z}}}$

- * Instantaneous Power : $P = V \times i$



$$\Rightarrow P = V_m \sin \omega t \cdot i_m \sin (\omega t - \theta)$$

$$\Rightarrow P = \frac{V_m}{\sqrt{2}} \cdot \frac{i_m}{\sqrt{2}} \cos \theta - \frac{1}{2} V_m i_m \cos (2\omega t - \theta)$$

(fluctuating power is zero for one cycle)

- * Avg Power $\Rightarrow \underline{\underline{P_{avg} = V_{rms} i_{rms} \cos \theta}}$

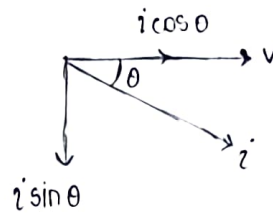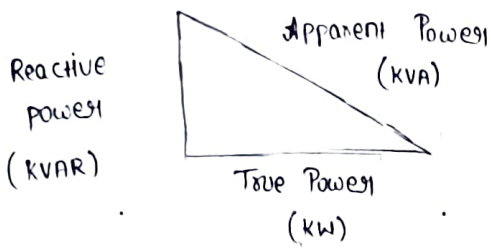→ Apparent Power, True Power, Reactive Power & Power factor:



* Apparent Power : $S = V_i = \frac{V_i}{1000} \times \frac{i \cos \theta}{1000}$
 KVA
 1000
 volt

* True Power (W)
 Real Power (W)
 Active Power
 $\Rightarrow P = V_i \cos \theta = \frac{V_i \cos \theta}{1000} \text{ (kW)}$
 watts

* Reactive Power $\Rightarrow Q = V_i \sin \theta = \frac{V_i \sin \theta}{1000} \text{ KVAR}$
 ↳ reactive

* $\text{KVA} = \sqrt{(\text{kW})^2 + (\text{KVAR})^2}$

* Real Power : (P) → The actual power consumed in an A.C circuit

* Reactive Power : The power absorbed by pure reactance

* Apparent Power (or) Total Power (S) : It is given by 'product of V_i


* Power factor : $\cos \theta = \frac{R}{Z} = \frac{V_i \cos \theta}{V_i}$
 ↳ real power
 ↳ app. power

* The max value of P.F. is 1
 min value of P.F. is 0

R-c Series circuit :

A circuit containing a resistance in series with a capacitance.
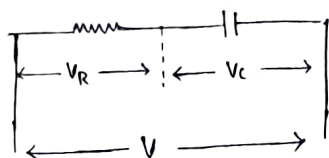
$$* V = \sqrt{V_R^2 + V_C^2} = i \sqrt{R^2 + X_C^2}$$




$$* \tan \theta = \frac{V_C}{V_R} = \frac{X_C}{R}$$

* Instantaneous voltage $\Rightarrow V = V_{\max} \sin \omega t$

ii current $\Rightarrow i = i_m \sin (\omega t + \theta)$

$$\therefore P = V i \cos \theta$$

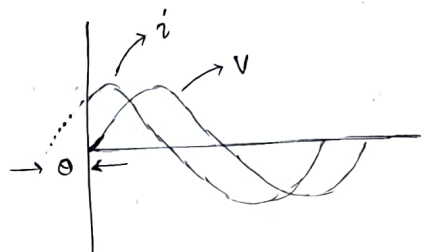

R-L-C Series circuit :


~~Case :~~

→ Conditions :



i) $X_L > X_C \rightarrow$ inductive

ii) $X_C > X_L \rightarrow$ capacitive


iii) $X_L = X_C \rightarrow$ Resistive.

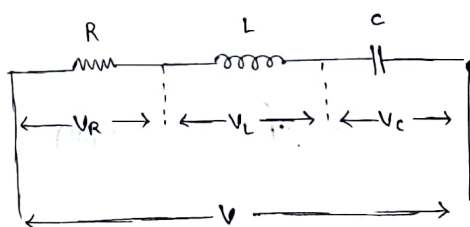


→ Case - 1 :

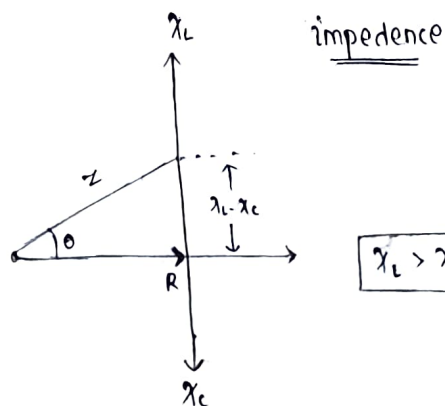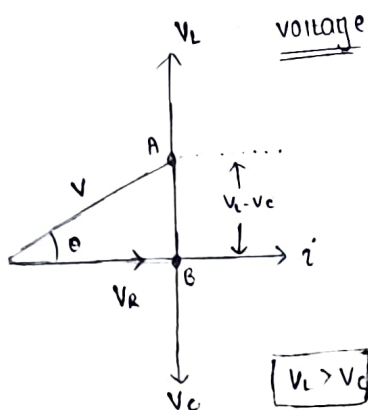

→ Case - 2 :

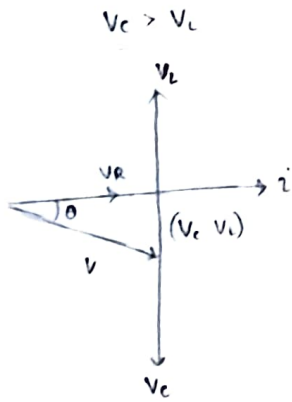


$\chi_c > \chi_L$

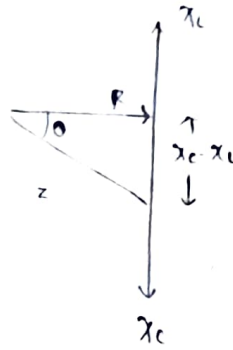

→ Case - 3 :

$\chi_L = \chi_c$

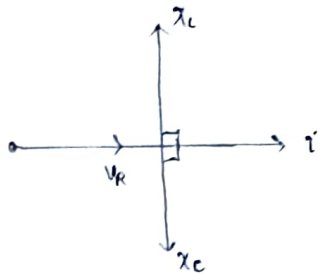

$(\chi_L - \chi_c) = 0$

* $\chi_L > \chi_c$ → Nature of circuit is inductive, so i lags the voltage
 $\theta > 0$ ($\theta \rightarrow$ phase angle)

* $\chi_c > \chi_L$ → Nature of circuit is capacitive, so i leads the voltage
 $\theta < 0$

* $\chi_c = \chi_L$ → Nature of circuit is resistive, i & v are in same phase
 $\theta = 0$