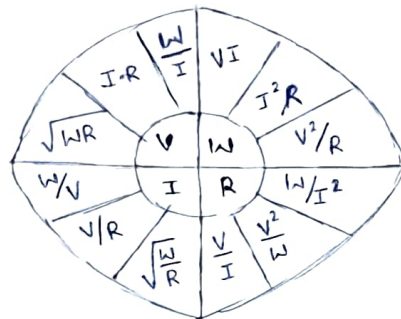


OHM'S LAW :

* The voltage across any specified conduction is directly proportional to the current flowing through it, when temperature remains same. $\therefore V \propto I$

$$\boxed{V = IR}$$



(Imp)





FORMULAE

KIRCHOFF'S LAWS :

→ KCL : The algebraic sum of all the currents meeting at a point/junction is zero. $\therefore \sum I = 0$

→ KVL : In a closed circuit, the sum of the potential drops is equal to the sum of the potential rises

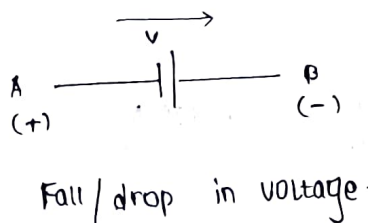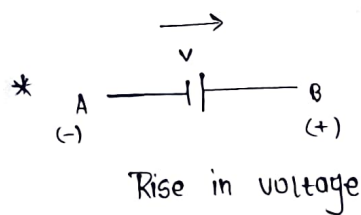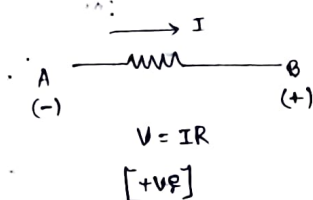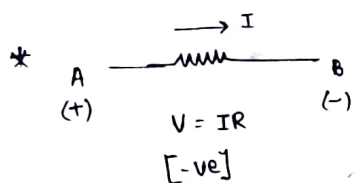DETERMINATION OF SIGNS FOR RESISTORS AND SOURCE :




* DC $\longrightarrow I, V$
 * AC $\longrightarrow i, v$ } Representation

\Rightarrow Find current i_e & i_D ?

Soln) KCL : $20 = 5 + 10 + i_e$

$$i_e = 5A$$

$$KCL : i_D = 5 + 10 + 5 = 20A$$

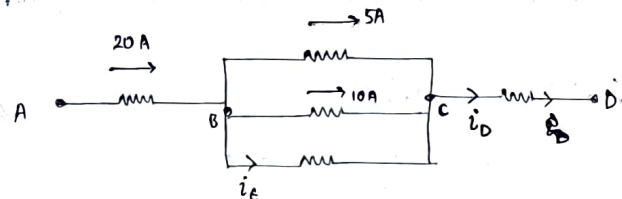

\Rightarrow Determine the missing voltage across the circuit :

Soln) Assume '0' V down
 \therefore they are at same junction.

Ans \rightarrow blue pen

\therefore Loop-1 : [KVL]


$$+100 - 40 - V_{BD} = 0$$

$$V_{BD} = 60V$$

Loop-2 : [KVL]

$$-20 + V_{BC} + V_{BD} = 0$$

$$V_{BC} = 40V$$

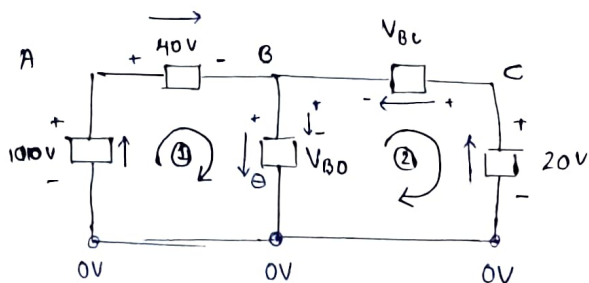

⇒ Determine the current i.e. flowing through 5Ω resistor?


Soln/ $400 - 230 = \underline{170V}$

$$V = iR$$

$$i = \frac{170}{5} = \underline{34 A}$$

$$P = Vi$$
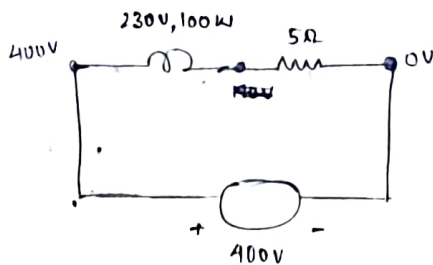
$$i = \frac{P}{V} = \frac{100}{230} = \underline{0.435 A}$$



⇒ An electric bulb is rated to 230V, 60W. Determine the current when current through the bulb & cost of energy for 30 days. If the bulb is switched on for 6 hrs per day. Assume electric energy cost 0.35/-/kWh. (1kWh = 1 unit)

Soln/ $P = Vi$

$$i = \frac{60}{230} = \underline{\underline{\frac{6}{23} A}}$$

$$W = Pt$$

$$W = (60)(6 \text{ hr}) = 360 \text{ Wh}$$

$$W = 6(360)(30) = 10800 \text{ Wh/hr}$$


$$\therefore \text{cost} = 10800 \times \frac{35}{100} \text{ W/hr}$$

$$= 3780 \text{ W/hr}$$

$$\underline{\underline{\text{Cost} = 3.7 \text{ kWh/hr (Ans)}}}$$

→ VERIFICATION OF KIRCHOFF'S LAW :

→ KCL :

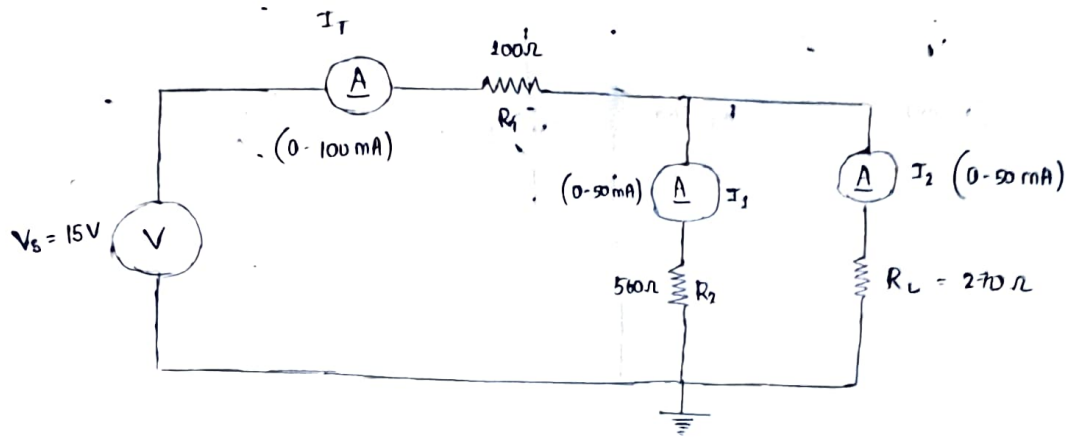


TABLES COLUMN :

V_s		I_T		I_1		I_2	
Theory	Practical	Theory	Practical	Theory	Practical	Theory	Practical
15V			54.2		17.6		36.6
			71.2		48.4		22.8

20V
 ✓
 o/p
 verified
 (B) hash.

→ KVL :



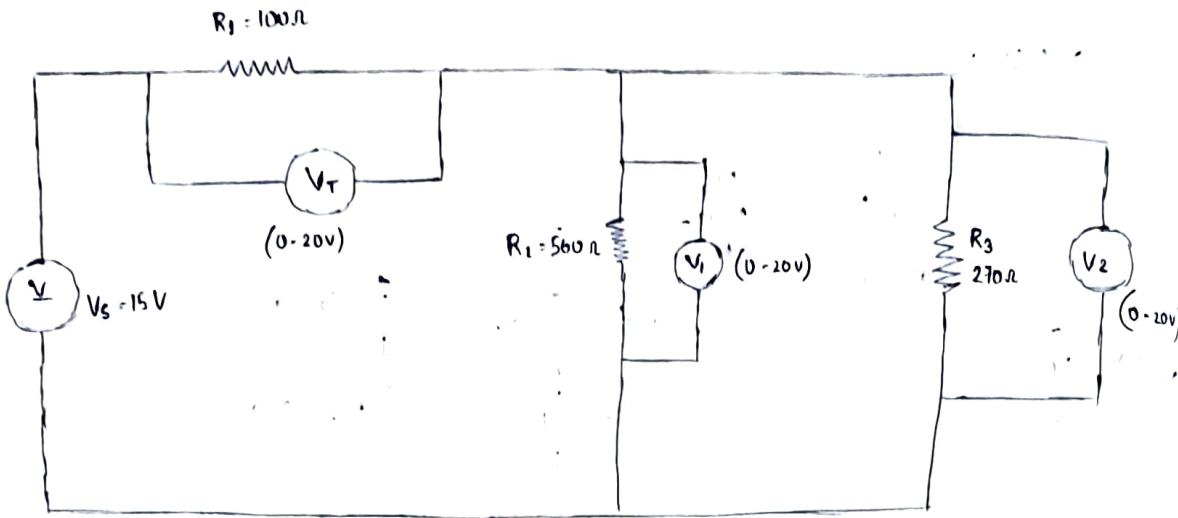


V_S	V_T		V_1		V_2	
	Theory	Practical	Theory	Practical	Theory	Practical
15V		4V		16V		10V
20V		6V		13V		13V

o/p
verified
B
hust.

⇒ Find the unknown resistance & current flowing through the circuit. Assume total power = 20W

Soln

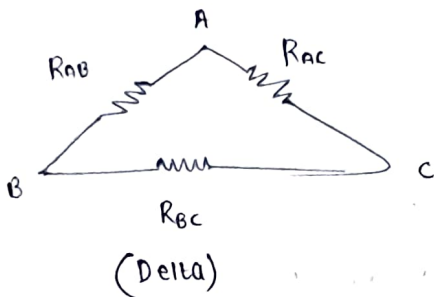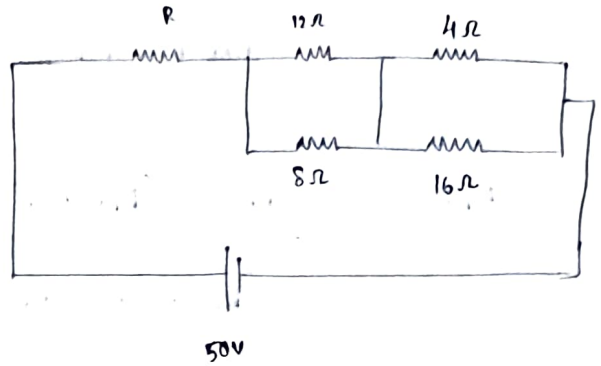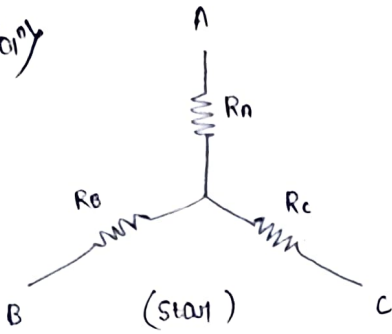

Δ to star, Y, (wye)

$R_A =$

* Derivation Δ to star, Y, (wye)

$$R_A + R_B = \frac{R_{AB} R_{CA} + R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B + R_C = \frac{R_{BC} (R_{AB} + R_{CA})}{R_{AB} + R_{AC} + R_{BC}} \rightarrow (2)$$

$$R_A + R_B = \frac{R_{AB} (R_{CA} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \rightarrow (1)$$

$$R_C + R_A = \frac{R_{CA} (R_{AB} + R_{BC})}{R_{AB} + R_{AC} + R_{BC}} \rightarrow (3)$$

$$(3) - (2)$$

$$R_A - R_B = \frac{R_{AB} R_{CA} - R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{AC}} \rightarrow (4)$$

$$(1) + (4)$$

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{AC}}$$

Similarly

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{AC}}$$

$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{BC} + R_{AC}}$$

* Start to Delta:

$$R_A R_B = \frac{(R_{AB})^2 (R_{CA} R_{BC})}{(R_{AB} R_{BC} + R_{CA})^2}$$

$$R_B R_C = \frac{(R_{BC})^2 (R_{AB} R_{CA})}{(R_{AB} + R_{AC} + R_{BC})^2}$$

$$R_C R_A = \frac{(R_{CA})^2 (R_{AB} R_{BC})}{(R_{AB} + R_{BC} + R_{AC})^2}$$

$$R_A R_B + R_B R_C + R_A R_C = \frac{R_{AB} R_{BC} R_{CA} (R_{AB} + R_{BC} + R_{CA})}{(R_{AB} + R_{BC} + R_{CA})^2}$$

$$R_A R_B + R_B R_C + R_A R_C = \frac{R_{AB} R_{BC} R_{CA}}{(R_{AB} + R_{BC} + R_{CA})}$$

$$R_A R_B + R_B R_C + R_C R_A = R_{AB} \cdot R_C$$

imp

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_{BC}} \Rightarrow a$$



imp

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_A}$$



imp

$$R_{AC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_B}$$

→ If all $R_{AB} = R_{BC} = R_{AC} = R$.

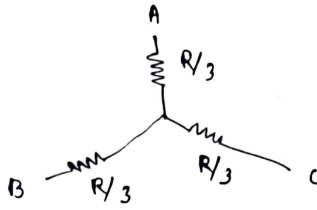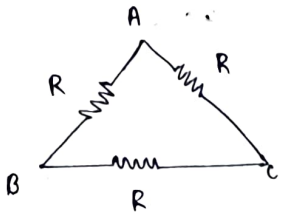

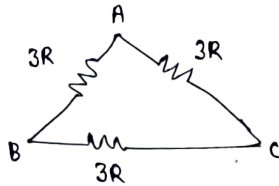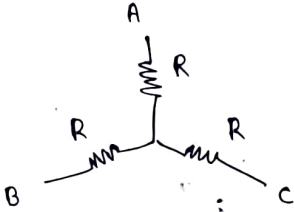→ Case - 2 : $Y \Rightarrow \Delta$, $R_A = R_B = R_C = R$.







⇒ Use Δ to Y : find equivalent resistance b/w A & B.

Solⁿ

$$R_1 = \frac{(4)(4)}{4+4+2} = \frac{16}{10} = 1.6 \Omega$$

$$R_2 = \frac{(2)(4)}{10} = 0.8 \Omega$$

$$R_3 = \frac{(2)(4)}{10} = 0.8 \Omega$$

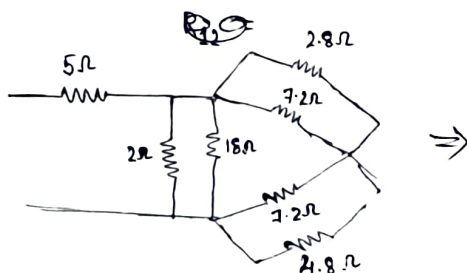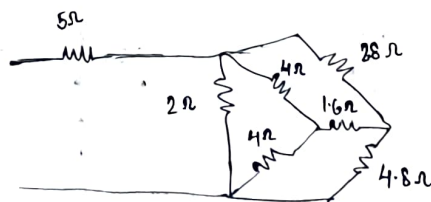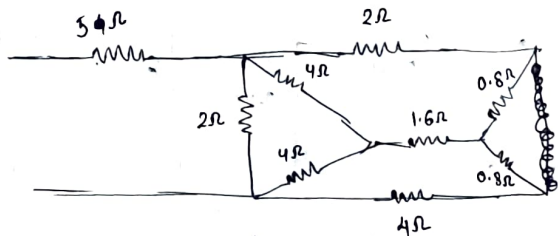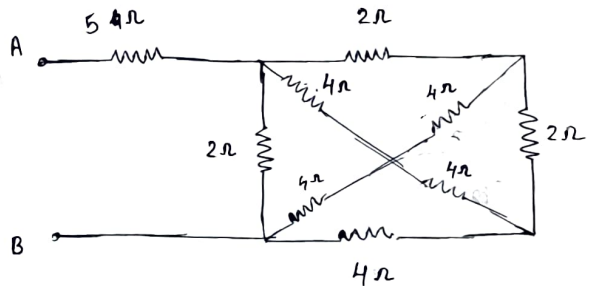

4Ω, 1.6Ω, 4Ω

are Y to Δ connected



$$R_1 = \frac{(4)(1.6) + (4)(1.6) + (4 \times 4)}{4}$$

$$R_1 = 7.2 \Omega$$

$$R_2 = 7.2 \Omega$$

$$R_3 = 18 \Omega$$



R

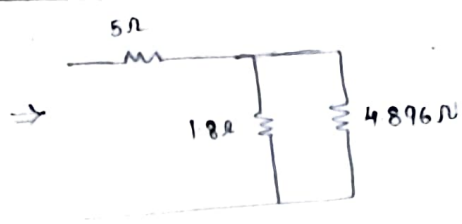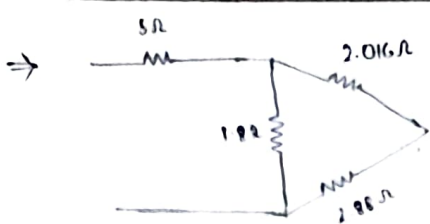


↓

(Ans)

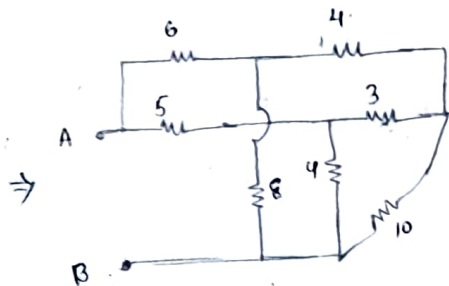
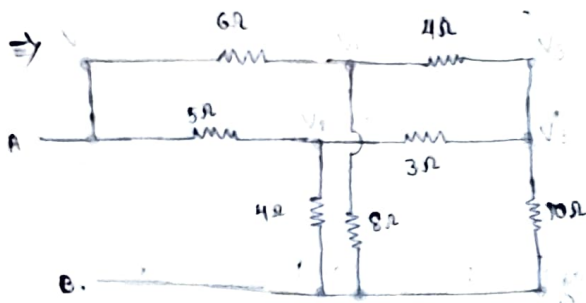
$$R_{eq} = 5 + \frac{(1.8)(4.896)}{(1.8) + (4.896)} = 6.316 \Omega$$




↓

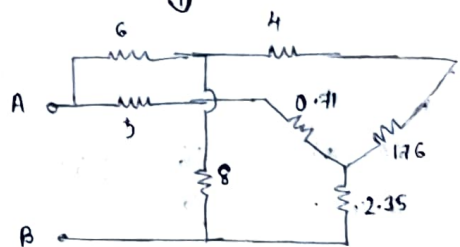


↓

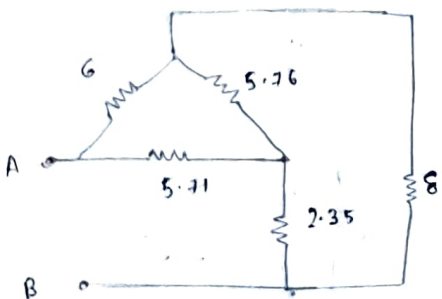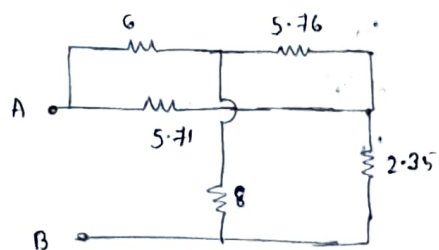


⇐

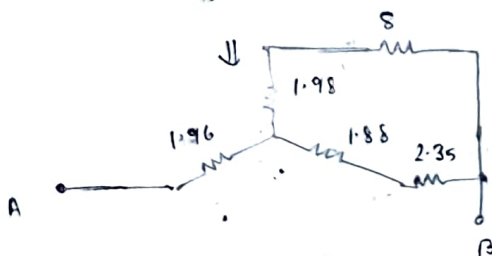

⇒

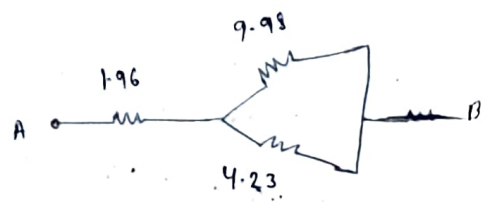

↓



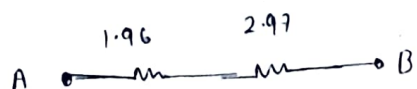


↓


$$R_{eq} = 4.93 \Omega$$

⇒ In the wheatstone bridge circuit shown in fig. Find the effective resistance b/w P & Q. Find the current supplied by 10V battery connected to PQ terminal.

Solⁿ

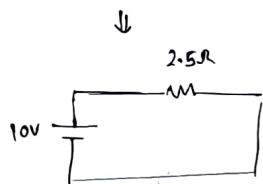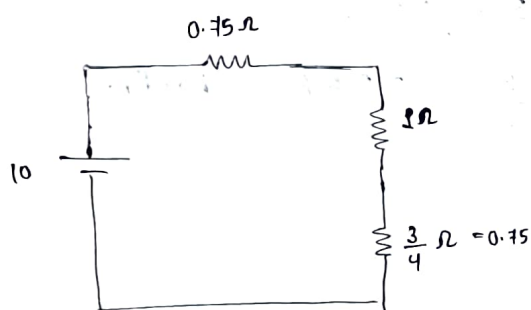
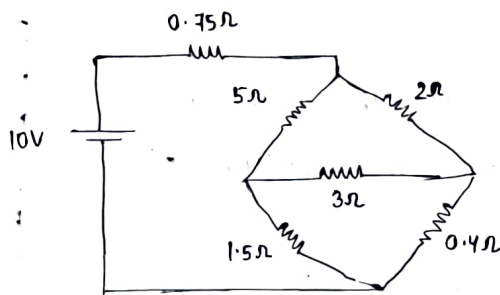

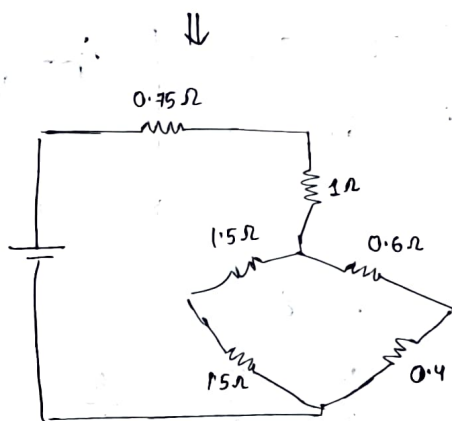
$$i = \frac{10}{2.5} = \frac{100}{25} = \underline{\underline{4A}}$$




$$\frac{3 \times 1}{3+1}$$

⇒ Find equiv resistance b/w A & B

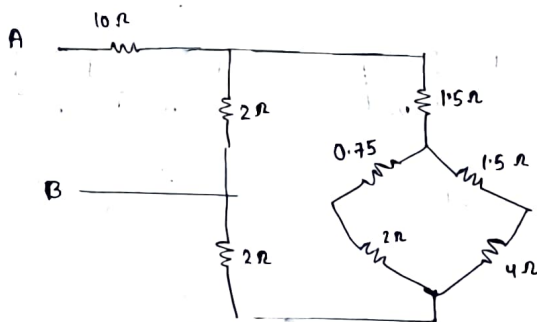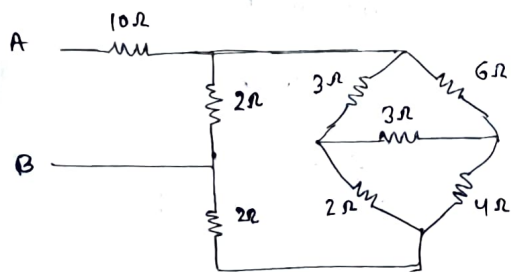

$$\underline{\underline{11.46 \Omega}}$$

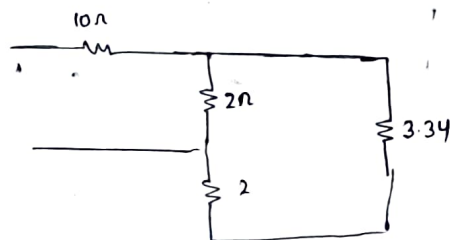

$$\frac{2.75 \times 6}{8.75}$$

$$\frac{1.89}{1.50}$$

$$8.39$$

$$5.34$$

2

⇒ Determine :

- i) The reading on ammeter
- ii) The value of resistor (R)


Solⁿ $11.5 = i_1 + 3 + i_3$

$i_1 + i_3 = 8.5$

$i_3 = 6 \text{ A}$



$V = 3 \times 5 = 15 \text{ V}$

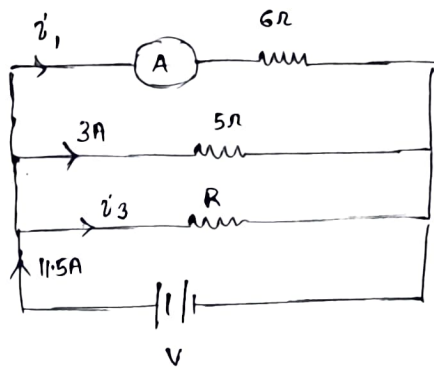$i_1 = \frac{15}{6} = \underline{\underline{2.5 \text{ A}}}$ (Reading)




ii) $R = \frac{V}{i_3} = \frac{15}{6} = \frac{5}{2} = \underline{\underline{2.5 \Omega}}$


Imp

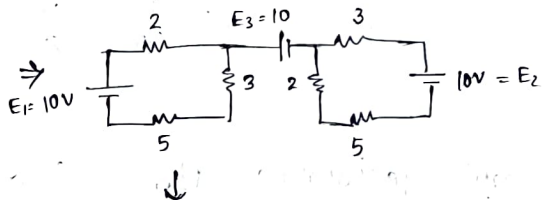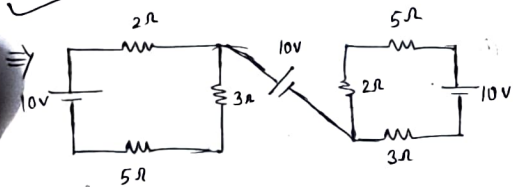



Solⁿ Consider E_1

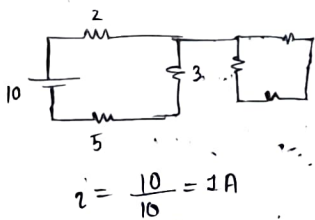

Consider E_2

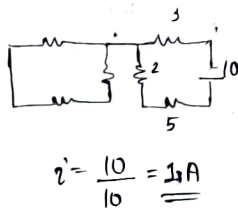

Consider E_3

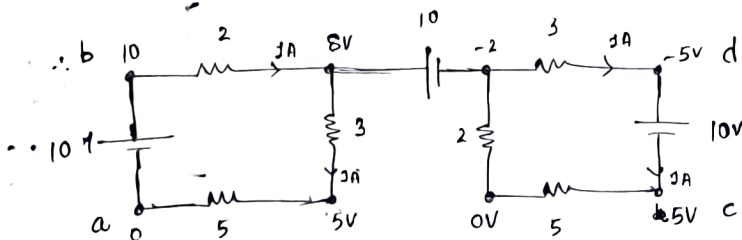
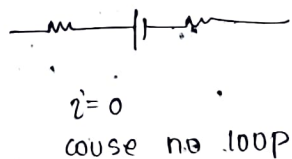


$\therefore V_{ad} = V_a - V_d = 0 - (-5) = \underline{\underline{5 \text{ V}}}$



$V_{bc} = V_b - V_c = 10 - 5 = \underline{\underline{5 \text{ V}}}$

SOURCE TRANSFORMATION :





→ Current Source to Voltage Source :

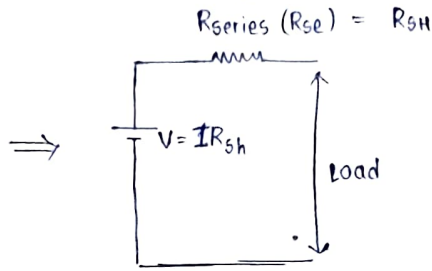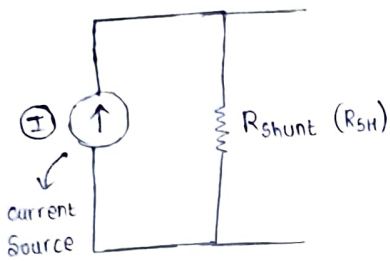

→ Voltage Source to Current Source :

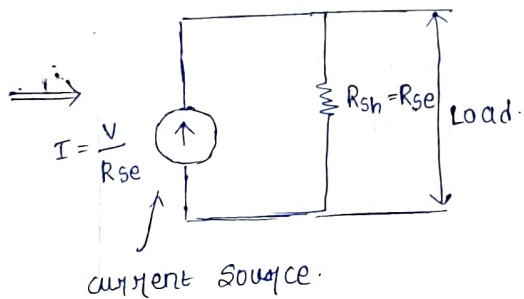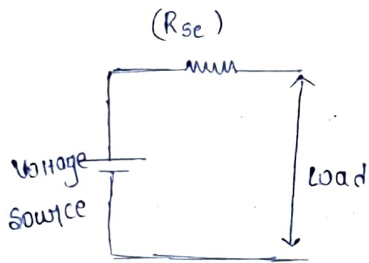


→ Example :

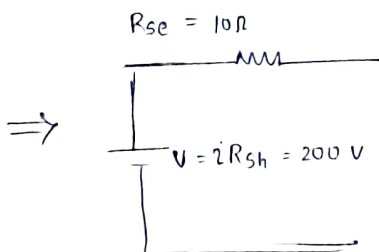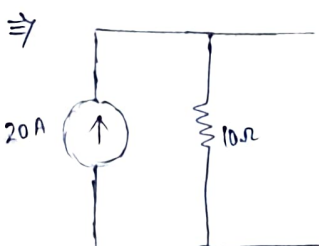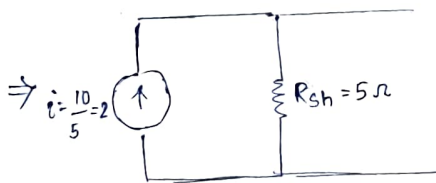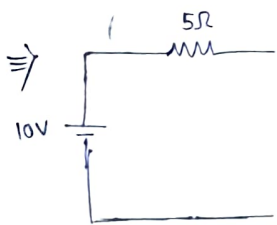

MESH / LOOP CURRENT METHOD :

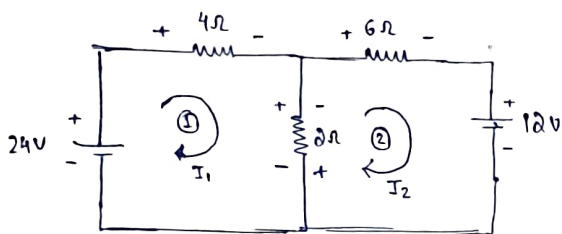⇒ Determine the current through various resistors using the concept of mesh current method ?



Sorry Always take dirⁿ of loop same.

then take sign on resistors according to dirⁿ of i

$$\textcircled{1} \rightarrow 24 - 4I_1 - 2I_1 = 0$$

$$I_1 = 4A$$

$$\textcircled{2} \rightarrow -6I_2 - 12 - 2I_2 = 0$$

$$8I_2 = -12$$

$$I_2 = \frac{-3}{2} = \underline{\underline{-1.5A}}$$

(wrong method).

$$\textcircled{1} \rightarrow 24 - 4I_1 - 2(I_1 - I_2) = 0$$

$$24 - 4I_1 - 2I_1 + 2I_2 = 0$$

$$24 = 6I_1 - 2I_2$$

$$\textcircled{2} \rightarrow -6I_2 - 12 - 2(I_2 - I_1) = 0$$

$$-6I_2 - 12 - 2I_2 + 2I_1 = 0$$

$$2I_1 = 8I_2 + 12$$

(correct method).

$$\therefore 24 = 6I_1 - 2I_2$$

$$2I_1 = 8I_2 + 12$$

$$\Rightarrow 8 = 8I_2 + 12 - \frac{2}{3}I_2$$

$$\Rightarrow -4 = \frac{22}{3}I_2$$

$$\Rightarrow I_2 = \frac{-12}{22} = \underline{\underline{-\frac{6}{11}A}}$$


$$I_1 = 4I_2 + 6$$

$$= \frac{-24}{11} + 6 = \underline{\underline{\frac{42}{11}A}}$$

$$\frac{24 - 2}{3}$$

⇒ In the

⇒ Determine the current in 8Ω resistor?

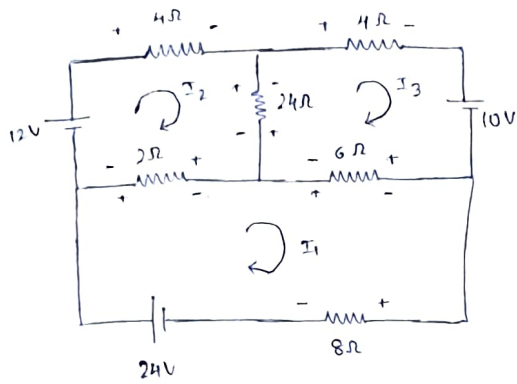

$$\begin{aligned} x &= I_1 \\ y &= I_2 \\ z &= I_3 \end{aligned}$$

Solⁿ ① $\rightarrow -4I_2 - (I_2 - I_3)24 - 2(I_2 - I_1) + 12 = 0$

$$-4I_2 - 24I_2 + 24I_3 - 2I_2 + 2I_1 + 12 = 0$$

$$\cancel{-6I_2} - 30I_2 + 24I_3 + 2I_1 + 12 = 0$$

② \rightarrow ~~③~~ $\rightarrow -4I_3 - 10 - 6(I_3 - I_1) - 24(I_3 - I_2) = 0$

$$-34I_3 + 6I_1 + 24I_2 - 10 = 0$$


① $\rightarrow 24 - 2(I_1 - I_2) - 6(I_1 - I_3) - 8I_1 = 0$

$$24 - 16I_1 + 2I_2 + 6I_3 = 0$$

$$\therefore \underline{\underline{i_1 = 2.06 \text{ A}}} \quad \underline{\underline{i_2 = 1.36}} \quad \underline{\underline{i_3 = 1.03 \text{ A}}}$$

MAXIMUM POWER TRANSFER THEOREM :

→ Thevenin's Theorem :

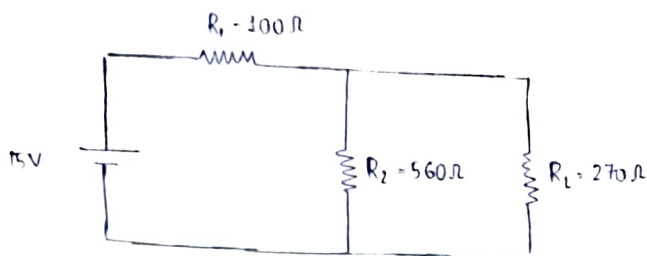

← Circuit diagram.

To solve this type of circuit :

* Step-1 : i) Find $V_{Th} = V_{oc}$

ii) Remove ' R_L ' & find voltage across ' R_L '


* Step-2 : i) Find R_{Th}

ii) Voltage source if present → Short circuit

Current source if present → Open circuit

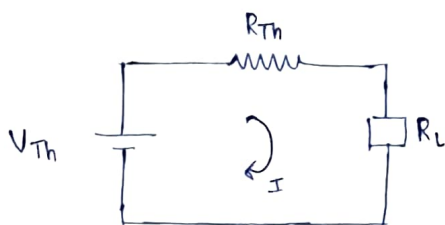
iii) View from ' R_L ' side & reduce the network & find R_{Th} .

* Step-3 : Draw equivalent circuit diagram




$$I = \frac{V_{Th}}{R_L + R_{Th}}$$

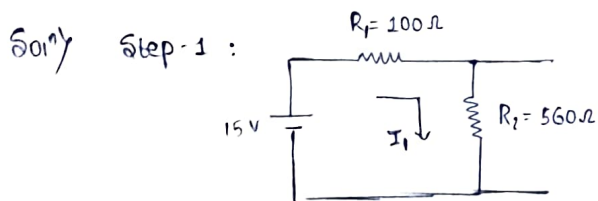Ex: Above circuit diagram. Solve using Thevenin's Theorem?




$$\therefore I_1 = \frac{V}{R_T} = \frac{15}{660} = 0.0227 \text{ A}$$

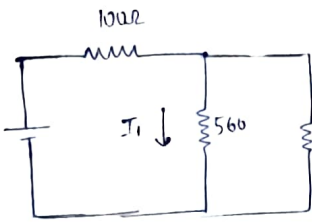Now put this I_1 in main circuit to get V_{Th}




$$V_{Th} = (0.0207) (560) = \underline{\underline{12.73 V}}$$

Step-2: Short circuit voltage source.

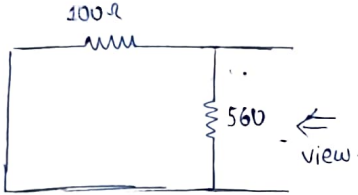

$$\Rightarrow R_{Th} = \frac{(100)(560)}{660} = \underline{\underline{84.84 \Omega}}$$

Step-3:

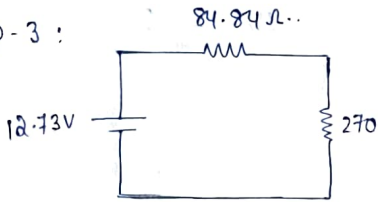


$$\Rightarrow i = \frac{V_{Th}}{R_{Th} + R_L} = \frac{12.73}{270 + 84.84} = \underline{\underline{0.0359 A}}$$

Assumed


S.No	R_L	R_{Th}	I_L	$P = I_L^2 R_L$
1	10	84.84	0.10196	0.4158
2	20	84.84	0.08788	0.4633
3	30	84.84	0.08085	0.4789
4	40	84.84	0.07182	0.4770
5	50	84.84	0.07301	0.4773
6	60	84.84	0.06088	0.4733
7	70	84.84	0.06239	0.4637
8	80	84.84	0.05661	0.4468

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

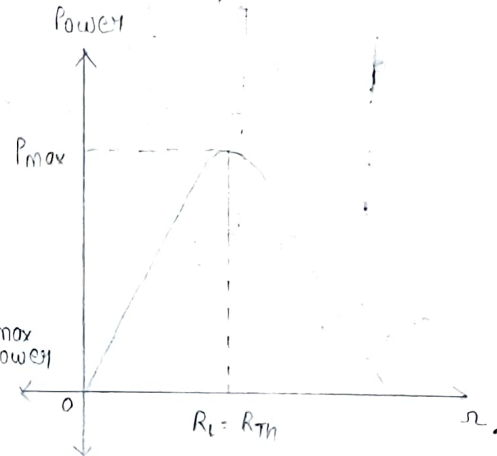

$$P_{max} \Rightarrow R_L = R_{Th}$$


Condition

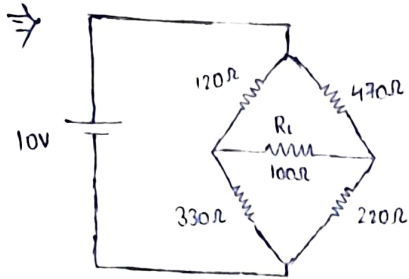

~~find~~

find max^m power?

Solⁿ

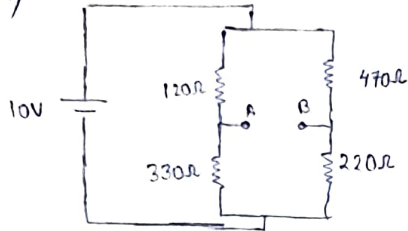


Step-1

voltage division.

$$\Rightarrow V_A = \left[\frac{330}{120 + 330} \right] \times 10 = \underline{\underline{7.33 \text{ V}}}$$


$$\Rightarrow V_B = \left[\frac{220}{470 + 220} \right] \times 10 = 3.188 \text{ V}$$
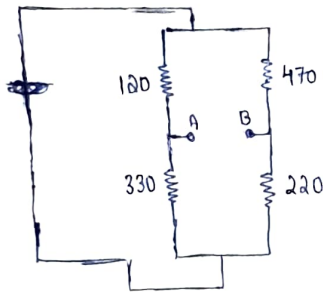
$$\therefore V_{Th} = 7.33 - 3.188 = \underline{\underline{4.1415 \text{ V}}}$$



Step-2

\Rightarrow

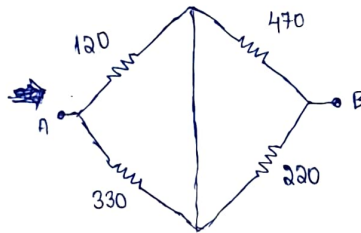


\Downarrow

$$R_{\text{left}} = \frac{330 \times 120}{330 + 120} = \frac{39600}{450} = 88 \Omega$$


$$R_{\text{right}} = \frac{470 \times 220}{470 + 220} = \frac{103400}{690} = 149.86 \Omega$$

\Downarrow

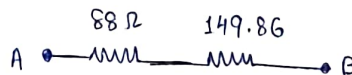

$$R_{Th} = \underline{\underline{237.86 \Omega}}$$

Step-3

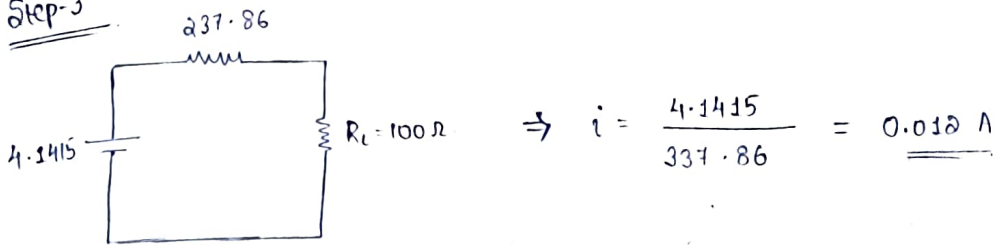


imp

$$\therefore P_{\max} = \frac{V_{Th}^2}{4 \cdot R_{Th}} = \frac{(4.1415)^2}{4(237.86)} = \underline{0.01803 \text{ W}}$$

(or to find P_{\max})

P_{\max} , when $R_{Th} = R_L$.

$$P_{\max} = \frac{V^2}{4R}$$

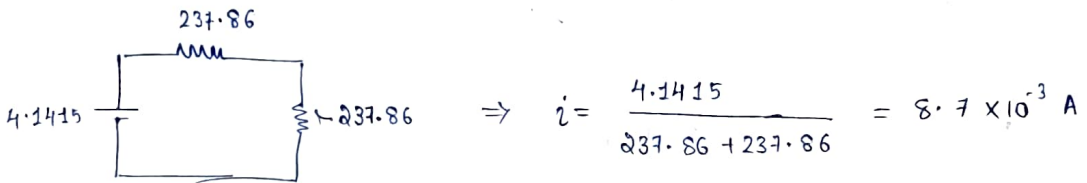


$$\therefore P_{\max} = Vi = (4.1415)(8.7 \times 10^{-3}) = 0.03603 \text{ W}$$

↑
This is for both
resistors.

$$\therefore \text{for only } R_L = \frac{0.03603}{2} = \underline{0.01803 \text{ W}}$$

$$(\text{or else}) \text{ use } P_{\max} = \frac{i^2 R}{8} = \frac{(4.1415)^2 (237.86)}{8} = \underline{0.01803 \text{ W}}$$

Network Reduction Method :

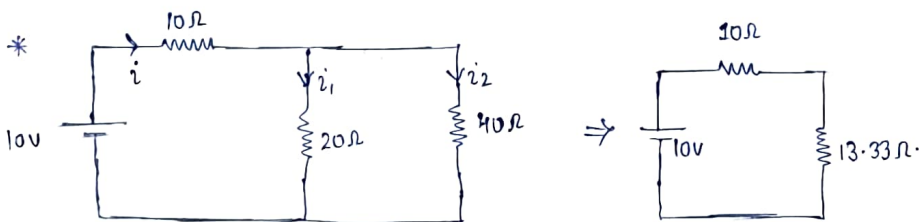


$$i = \frac{V}{R} = \underline{0.428 \text{ A}}$$

$$\therefore i_1 = \frac{i R_2}{R_1 + R_2} = \frac{(0.428)(40)}{60} = \underline{0.2857 \text{ A}}$$

$$i_2 = \frac{i R_1}{R_1 + R_2} = \frac{(0.428)(20)}{60} = \underline{0.1428 \text{ A}}$$

Loop ANALYSIS [USING CRENERS Rule]

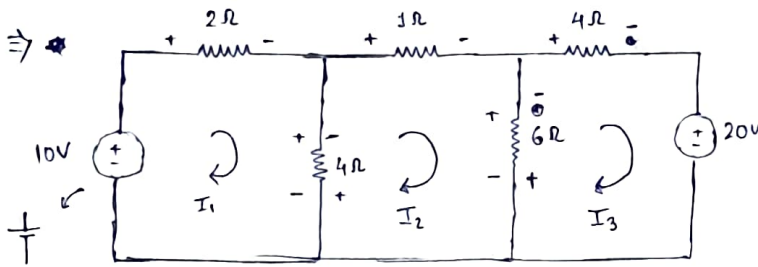

Find current in 6Ω ?

Soln

$$\begin{aligned} -2I_1 - 4I_1 + 10 &= 0 & -2I_1 - 4(I_1 - I_2) + 10 &= 0 \\ -1I_2 - 6I_2 - 4I_2 &= 0 & -1I_2 - 6(I_2 - I_3) - 4(I_2 - I_1) &= 0 \\ -4I_3 - 20 - 6I_3 &= 0 & -4I_3 - 20 - 6(I_3 - I_2) &= 0 \end{aligned}$$

Use determinant method to solve :

$$\Delta = \begin{bmatrix} 6 & -4 & 0 \\ 4 & -11 & 6 \\ 0 & 6 & -10 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 20 \end{bmatrix}$$

~~A x B~~

$$\begin{aligned} x &= \frac{D_1}{D} \\ y &= \frac{D_2}{D} \\ z &= \frac{D_3}{D} \end{aligned} \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{use this}$$

$$\Delta = 6 [110 - 36] + 4 [-40 - 0] + 0 [-] =$$


$$\therefore I_1 = 0.92 \text{ A}$$

$$I_2 = -1.13 \text{ A}$$

$$I_3 = -2.68 \text{ A}$$

$$\begin{aligned} \therefore i_{6\Omega} &= I_2 - I_3 = -1.1267 - (-2.676) \\ &= \underline{\underline{1.5493 \text{ A}}} \end{aligned}$$

NODAL ANALYSIS :

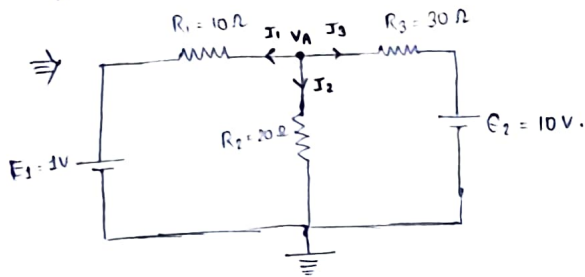

Ans with black pen.

So^{ny} $I_1 = \frac{V_A - 1}{10}$, $I_2 = \frac{V_A - 0}{20}$, $I_3 = \frac{V_A - 10}{30}$

using KCL :


$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_A - 1}{10} + \frac{V_A}{20} + \frac{V_A - 10}{30} = 0$$


$$6V_A - 6 + 3V_A + 2V_A - 20 = 0$$

$$11V_A = 26$$


$$V_A = \frac{26}{11} = 2.36$$

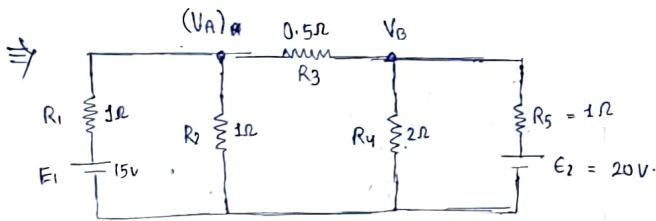

So^{ny} converting v source to i source.

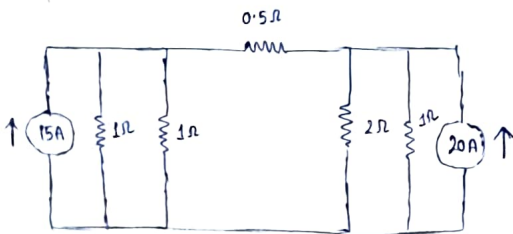

⇒

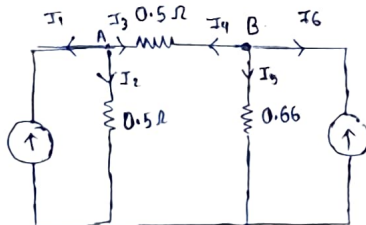

$$I_4 = \frac{V_B - V_A}{0.5} , I_5 = \frac{V_B}{0.66} , I_6 = -20$$

$$\frac{V_B}{0.5} - \frac{V_A}{0.5} + \frac{V_B}{0.66} - 20 = 0$$

$$2V_A - 3.5V_B = -20$$

$$\therefore V_A = 9.25V$$

$$V_B = 11V \quad \text{Ans}$$

$$I_1 = -15A$$


$$I_2 = \frac{V_A}{0.5} , I_3 = \frac{V_A - V_B}{0.5}$$

$$KCL = -15 + \frac{V_A}{0.5} + \frac{V_A - V_B}{0.5} = 0$$

$$2V_A - V_B = 15$$


$$4V_A - 2V_B = 30$$

SUPERPOSITION THEOREM :

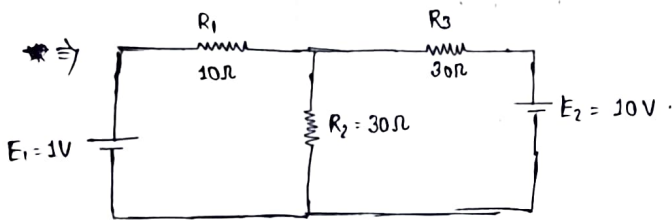


Find the current through R_2 .

Solⁿ Case - 1 : [considering E_1]

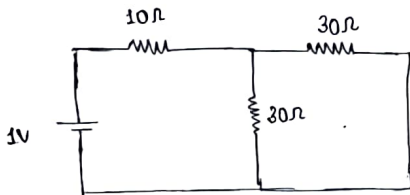

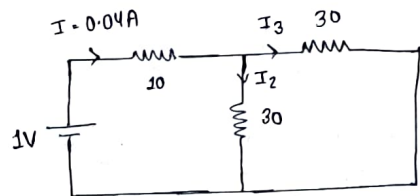
$$\Rightarrow I = \frac{1}{25} = \underline{\underline{0.04 \text{ A}}}$$




$$\therefore i_2 = (0.04) \left(\frac{30}{30+30} \right) = \underline{\underline{0.02 \text{ A}}}$$

$$i_3 = \underline{\underline{0.02 \text{ A}}}$$

Case - 2 : [considering E_2]

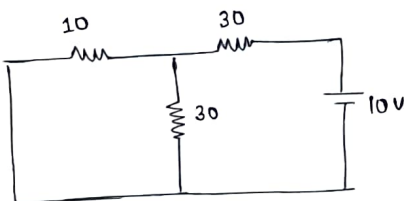
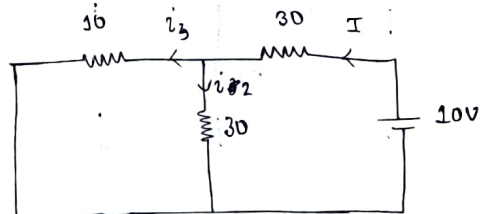
$$\Rightarrow i = \frac{10}{37.5} = \underline{\underline{0.267 \text{ A}}}$$




$$i_2 = (0.267) \left(\frac{10}{40} \right) = \underline{\underline{0.067 \text{ A}}}$$

$$\therefore i \text{ through } R_2 = 0.02 + 0.067 = \underline{\underline{0.087 \text{ A}}}$$

⇒ Find i through the branch A & B, using superposition theorem?

Soln/


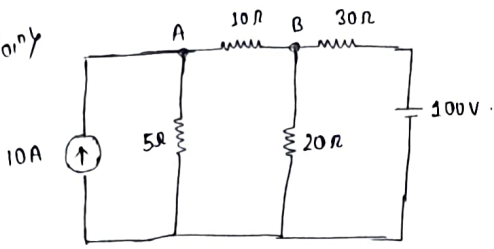


$$I_{AB} = 1.95185 \text{ A}$$

$$I_{BA} = 1.48148$$


$$I_T = 0.3703$$

Case - 1 [considering current source].

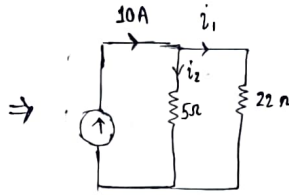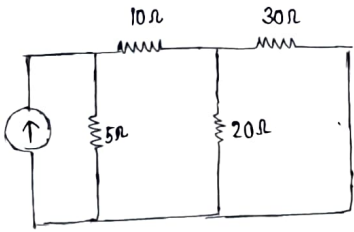


$$i_{s1} = (10) \left[\frac{5}{27} \right] = \underline{\underline{1.85185 \text{ A}}}$$

Case - 2

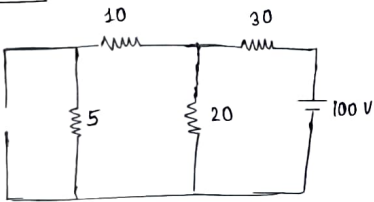

⇒

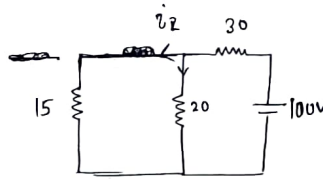

$$i = 38.5714 \text{ A}$$


$$\therefore i_2 = (38.5714) \left[\frac{20}{20 + 15} \right] = \underline{\underline{1.48148 \text{ A}}}$$

$$\therefore i_{AB} = i - i_2 = 1.85185 - 1.48148 = \underline{\underline{0.37037 \text{ A}}}$$


⇒ Find V_{Th} , R_{Th} & draw equiv. circuit.

Soln/ Voltage div. method.
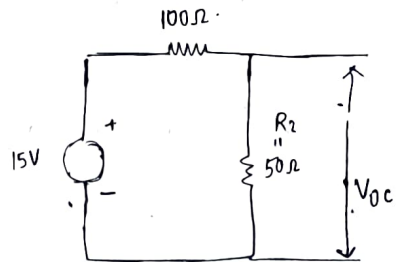
$$V_{R_2} = \left[\frac{50}{100 + 50} \right] [15] = \underline{\underline{5V}}$$




loop current method.

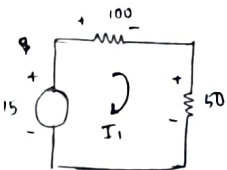

$$15 - 100I_1 - 50I_1 = 0$$
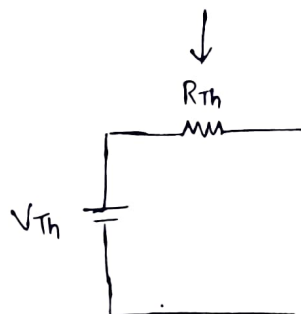
$$\therefore I_1 = 0.1 \text{ A} \quad \therefore V_{R_1} = 5V \text{ (Ans)}$$



~~Vol~~MAXIMUMPOWERTHEOREM

Voltage

 V_{Th} R_{Th}

I

Theo

 P_{pac}

Theo

Pract

Theo

 P_{pac}

15V

12.13V

12.60V

84.80 Ω 84.50 Ω

35.9mA

36.5mA

 $R_L (\Omega)$ $R_{Th} (\Omega)$ $I_L (mA)$ $P = I_L^2 R_L$

50

84.5

94.7

448 W

60

84.5

88.1

465.69 W

70

84.5

82.3

474.13 W

80

84.5

77.1

475.55 W

84.5

84.5

75.6

482.94 W

90

84.5

72.6

474.36 W

100

84.5

69.5

469.22 W

110

84.5

65.7

464.21 W

120

84.5

62.3

465.75 W

130

84.5

59.5

460.23 W

