
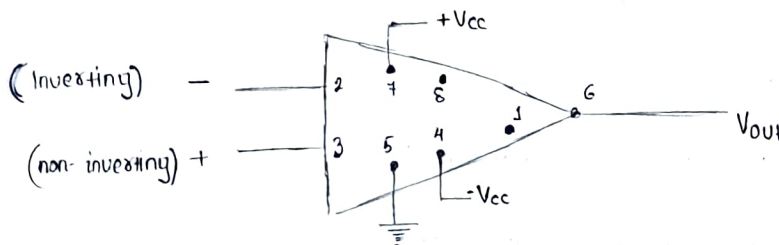


OPERATIONAL AMPLIFIER [OP AMP]

* An operational amplifier is a direct coupled, high gain, amplifier with feedback. It is commonly known as 'opamp'.

This is called so because of its ability to perform mathematical operations such as addition, int., diff., etc.

→ Block diag. of opamp:

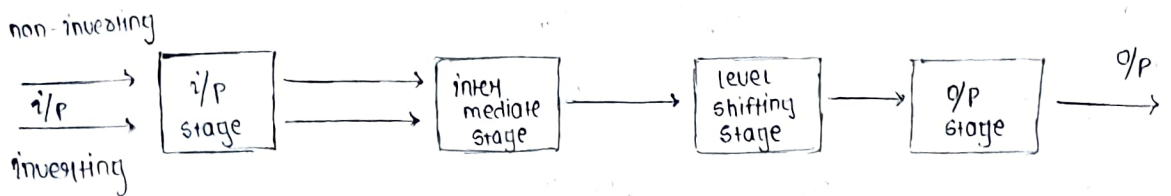

opamp
in
diagram

* Input stage:

It is a dual i/p, double ended o/p differential amplifier.

It has highest gain

* Intermediate stage:

It is a dual i/p, single ended o/p differential amplifier.

It also provides some amplification.

* Level shifting stage:

It is an emitter follower circuit. It shifts the o/p of intermediate stage to zero dc voltage w.r.t ground.

* Output stage :

It is a push pull complementary amplifier to raise the current supplying capacity, to increase o/p voltage ~~drift~~ swing and to provide low o/p resistance.

→ Properties of an ideal opamp :

- * open loop voltage gain is infinity ($A_v = \infty$)
- * A large voltage gain when operating without feedback
- * Input impedance is infinity ($Z_{in} = \infty$)
- * o/p impedance is zero ($Z_{out} = 0$)
- * Bandwidth is infinity ($BW = \infty$)
- * Common mode rejection ratio is infinity ($CMRR = \infty$)
- * Slow rate is ∞
- * Perfect balance is $V_o = 0$, when $V_1 = V_2$
- * Characteristics do not vary with temperature.
- * Voltage gain remains constant over a wide freq. range.

→ Slow rate of opamp :

It is defined as the max rate of change of o/p voltage per unit of time. It is expressed in volts/microsecond.

$$SR = \left(\frac{dV_o}{dt} \right)_{\max} \text{ V}/\mu\text{sec.}$$

→ Open loop gain of opamp :

open loop gain (A_v) of an opamp is the ratio of o/p voltage (V_o) to the differential i/p voltage (V_{id}) without feed back.


$$A_v = \frac{V_o}{V_{id}}$$

→ CMRR of an opamp :

It is a measure of ability of opamp to suppress the common mode signals. It is defined as ratio of differential mode gain to the common mode gain

$$CMRR = \frac{\text{Diff. mode gain}}{\text{Common mode gain}} = \frac{A_d}{A_{cm}}$$

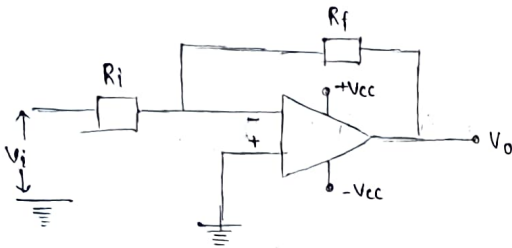→ Circuit diagram of an inverting amplifier and its o/p expression.




$$V_o = -\frac{R_f}{R_i} \cdot V_i$$

Gain of inverting amplifier :


$$\text{Gain } A_{v_f} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

where R_f = feed back resistance

R_i = i/p resistance

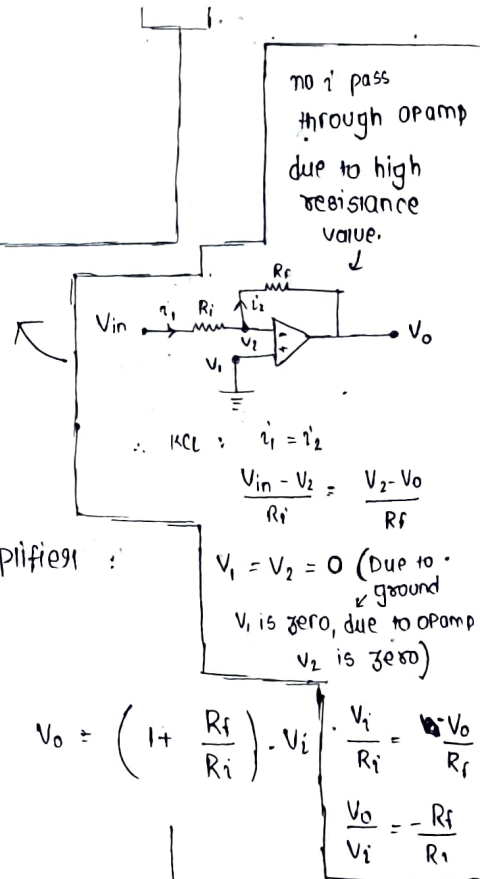

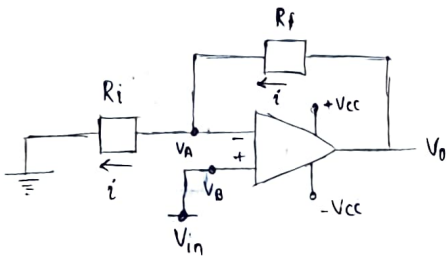→ Circuit diag. of a non-inverting amplifier :



$$V_o = \left(1 + \frac{R_f}{R_i}\right) \cdot V_i$$

$$\frac{V_o}{V_i} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

Gain expression : $A_{v_f} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$

$$V_{in} = V_A = V_B, \quad i = \frac{V_o - V_A}{R_f} = \frac{V_o - V_{in}}{R_f}$$

$$i = \frac{V_A - 0}{R_i}$$

$$i = i$$

$$\frac{V_o}{R_f} - \frac{V_{in}}{R_f} = \frac{V_{in}}{R_i} \Rightarrow \frac{V_o}{R_f} = V_{in} \left[\frac{1}{R_f} + \frac{R_f}{R_i} \right] \Rightarrow V_o = \left[1 + \frac{R_f}{R_i} \right] V_{in}$$

Investing

* Input voltage is applied to investing terminal of opamp through R_i

* Voltage shunt feedback is used

* The o/p is phase reversed.

* Gain : $A_{vf} = -\frac{R_f}{R_i}$

⇒ Draw the ckt diagram of non-inverting amplifier with a feedback gain of 30

Soln


$$A_{vf} = 30$$

$$1 + \frac{R_f}{R_i} = 30$$

$$R_f = 29 R_i$$

Assume, $R_i = 10 \text{ k}\Omega$

$$R_f = 290 \text{ k}\Omega$$

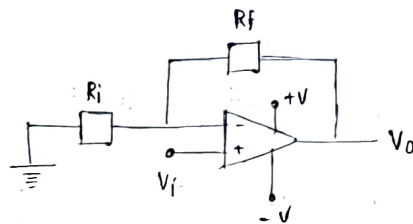

⇒ Design a ckt using opamp to get an o/p of 6V from an i/p of 2V

Soln

$$V_o = 6\text{V}, \quad V_i = 2\text{V}$$

$$R_f = ?$$

for non-inverting amplifier.

$$V_o = \left(1 + \frac{R_f}{R_i}\right) \cdot V_i$$

$$R_f = 2 R_i$$

Assume, $R_i = 10 \text{ k}\Omega$

$$R_f = 20 \text{ k}\Omega$$

Non-inverting

* Input voltage is directly applied to non-inverting terminal of opamp.

* Voltage series feedback is used

* The o/p is inphase with the i/p

* Gain : $A_{vf} = \left(1 + \frac{R_f}{R_i}\right)$