

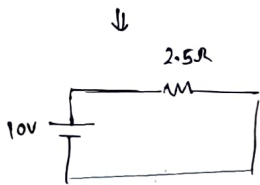
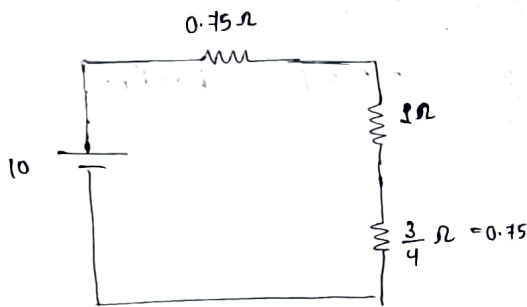


⇒ In the wheatstone bridge circuit shown in fig. Find the effective resistance b/w P & Q. Find the current supplied by 10V battery connected to PQ terminal.

Sol<sup>n</sup>


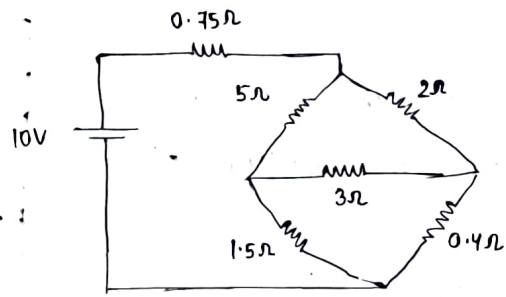

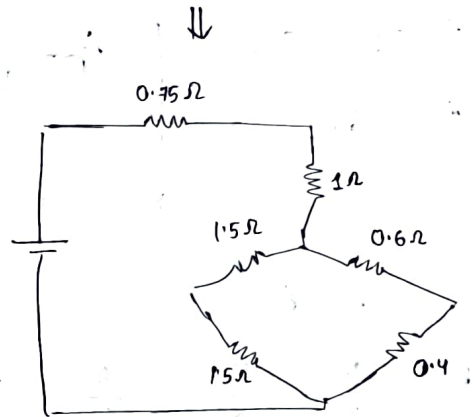
$$i = \frac{10}{2.5} = \frac{100}{25} = \underline{\underline{4A}}$$




$$\frac{3 \times 2}{3+1}$$

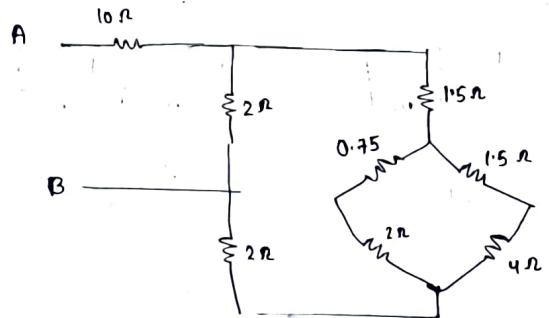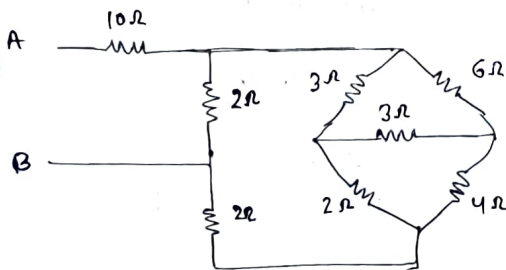⇒ Find equiv<sup>n</sup> resistance b/w A & B



$$\underline{\underline{11.46 \Omega}}$$

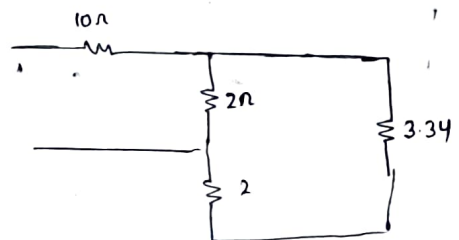


$$\frac{2.75 \times 6}{8.75}$$

$$\frac{1.89}{1.50}$$


$$\frac{3}{124}$$

$$\frac{5.34}{2}$$

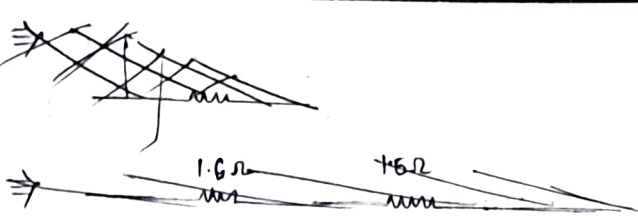

⇒ Determine :

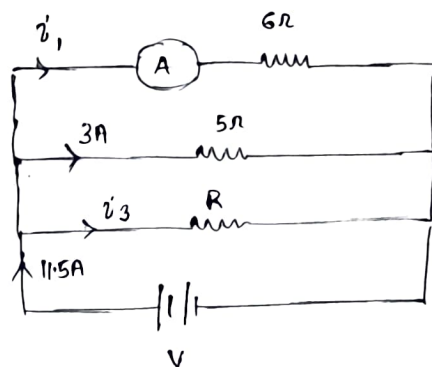- i) The reading on ammeter
- ii) The value of resistor (R)



Sol<sup>n</sup>  $11.5 = i_1 + 3 + i_3$

$$i_1 + i_3 = 8.5$$



$$i_3 = 6A$$

$$V = 3 \times 5 = 15V$$


$$i_1 = \frac{15}{6} = 2.5A \text{ (Reading)}$$

ii)  $R = \frac{V}{i_3} = \frac{15}{6} = \frac{5}{2} = 2.5\Omega$

Imp

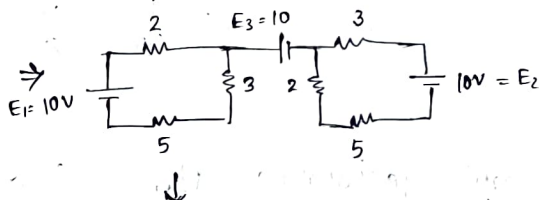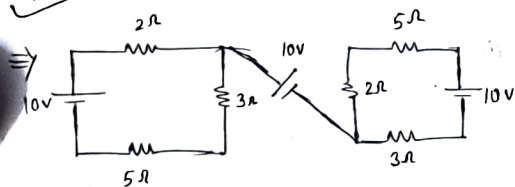


Sol<sup>n</sup> Consider  $E_1$

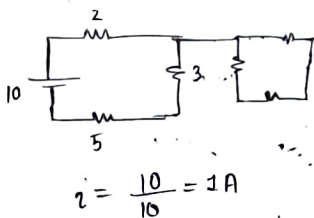


$$i = \frac{10}{10} = 1A$$

Consider  $E_2$

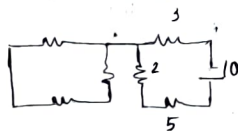


$$i = \frac{10}{10} = 1A$$

Consider  $E_3$

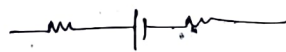

$i = 0$   
cause no loop


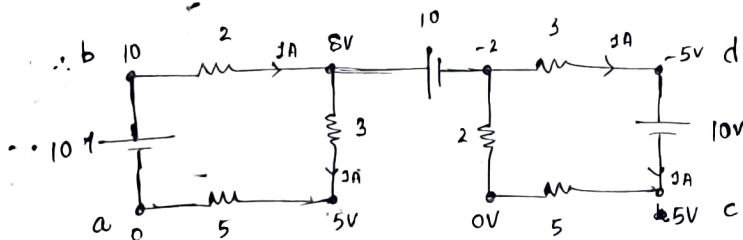


$$\therefore V_{ad} = V_a - V_d = 0 - (-5) = 5V$$



$$V_{bc} = V_b - V_c = 10 - 5 = 5V$$

# # SOURCE TRANSFORMATION :





→ Current Source to Voltage Source :

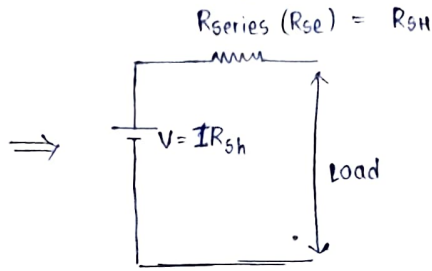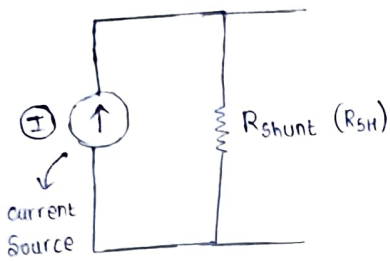

→ Voltage Source to Current Source :

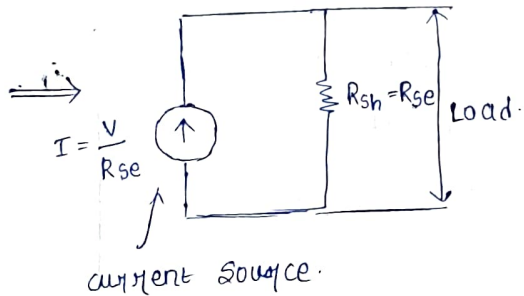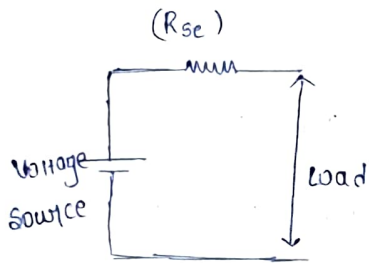


→ Example :

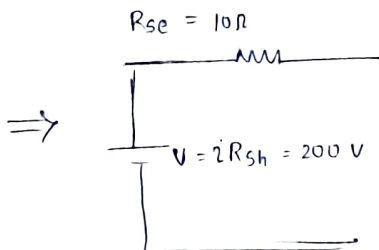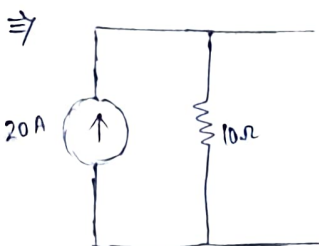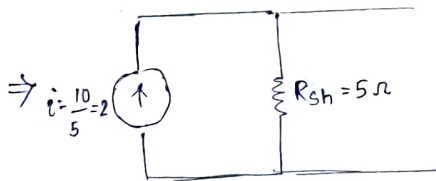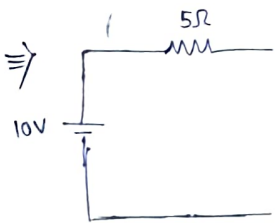
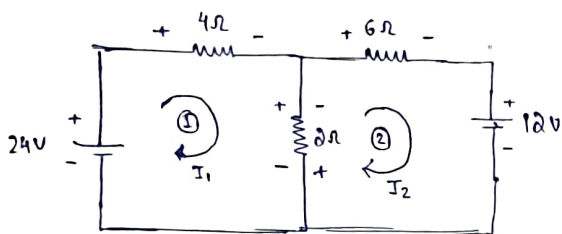
# # MESH / LOOP CURRENT METHOD :

⇒ Determine the current through various resistors using the concept of mesh current method ?



So, always take dir<sup>n</sup> of loop same.

then take sign on resistors according to dir<sup>n</sup> of i

$$\textcircled{1} \rightarrow 24 - 4I_1 - 2I_1 = 0$$

$$I_1 = 4A$$

$$\textcircled{2} \rightarrow -6I_2 - 12 - 2I_2 = 0$$

$$8I_2 = -12$$

$$I_2 = \frac{-3}{2} = \underline{\underline{-1.5A}}$$

(wrong method).

$$\textcircled{1} \rightarrow 24 - 4I_1 - 2(I_1 - I_2) = 0$$

$$24 - 4I_1 - 2I_1 + 2I_2 = 0$$

$$24 = 6I_1 - 2I_2$$

$$\textcircled{2} \rightarrow -6I_2 - 12 - 2(I_2 - I_1) = 0$$

$$-6I_2 - 12 - 2I_2 + 2I_1 = 0$$

$$2I_1 = 8I_2 + 12$$

(correct method).

$$\therefore 24 = 6I_1 - 2I_2$$

$$2I_1 = 8I_2 + 12$$

$$\Rightarrow 8 = 8I_2 + 12 - \frac{2}{3}I_2$$

$$\Rightarrow -4 = \frac{22}{3}I_2$$

$$\Rightarrow I_2 = \frac{-12}{22} = \underline{\underline{-\frac{6}{11}A}}$$

$$I_1 = 4I_2 + 6$$

$$= \frac{-24}{11} + 6 = \underline{\underline{\frac{42}{11}A}}$$

$$\frac{24 - 12}{3}$$