

DIGITAL CIRCUITS / LOGIC CIRCUITS

LOGIC GATES :

→ Not Gates : $x \rightarrow \neg x$

Truth Table

Boolean eqⁿ

x	y
0	1
1	0

$$y = \bar{a} \text{ or } \bar{x}$$

→ AND Gate : $a, b \rightarrow y$

↓

2^n tables

where $n \rightarrow$ no. of inputs

a	b	y
0	0	0
0	1	0
1	0	0
1	1	1

$$y = a \cdot b$$

→ OR Gate : $a, b \rightarrow y$

a	b	y
0	0	0
0	1	1
1	0	1
1	1	1

$$y = a + b$$

→ NAND Gate : $a, b \rightarrow y$

a	b	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{a \cdot b}$$

→ NOR Gate : $a, b \rightarrow y$

a	b	y
0	0	1
0	1	0
1	0	0
1	1	0

$$y = \overline{a + b}$$

→ XOR Gate : $a, b \rightarrow y$

a	b	y	y'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$y = A \oplus B$$

$$ab + \bar{a}\bar{b}$$

$$a\bar{b} + \bar{a}b$$

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$\overline{A \oplus B} = AB + \bar{A}\bar{B}$$

→ XNOR Gate : $a \oplus b = y$

a	b	y
0	0	1
0	1	0
1	0	0
1	1	1


$$y = \overline{A \oplus B}$$

* NOT
AND
OR } Basic Gates


NAND
NOR
~~XOR~~
~~XNOR~~ } Desired Gates
(only)
Universal Gates.

⇒ Generate OR operation using 3 NAND Gates ?

Solⁿ

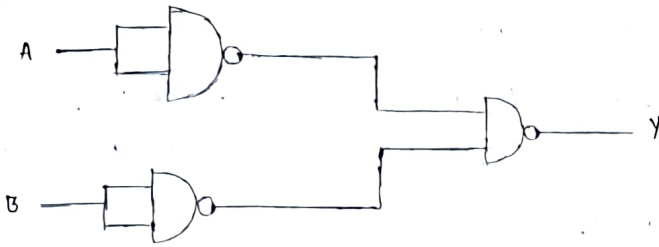
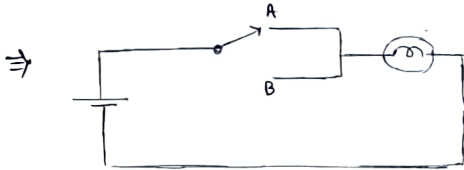
$$\therefore Y = \overline{\overline{A} \cdot \overline{B}} = \underline{\underline{A+B}}$$



Solⁿ for lamp on → 1
for lamp off → 0.

A	B	y
0	0	0 → not possible
1	0	1
0	1	1
1	1	0 → not possible

XOR circuit ←

⇒ Convert (37) decimal to binary :

$$\begin{array}{r} 18 \\ 2 \overline{) 37} \\ \underline{36} \\ 1 \end{array} \rightarrow 1 \text{ LSD}$$

↳ least significant digit

$$\begin{array}{r} 2 \\ 2 \overline{) 4} \\ \underline{4} \\ 0 \end{array} \text{ LSD}$$

$$\begin{array}{r} 1 \\ 2 \overline{) 2} \\ \underline{2} \\ 0 \end{array} \text{ LSD}$$

$$\begin{array}{r} 4 \\ 2 \overline{) 9} \\ \underline{8} \\ 1 \end{array} \text{ LSP}$$

$$\begin{array}{r} 0 \\ 2 \overline{) 1} \\ \underline{0} \\ 1 \end{array} \text{ MSD} \rightarrow \text{Max significant digit}$$

∴ ~~101001~~

(100101)₂ → start from down.

⇒ Convert 0.95 to its binary equivalent?

Soln	Fraction	Radix	Result	Recorded Carriers.
	0.95	2	$(0.95 \times 2) = 1.9$ ↓ 1 + 0.9	1
	0.9	2	1.8 → 1 + 0.8	1
	0.8	2	1.6 → 1 + 0.6	1
	0.6	2	1.2 → 1 + 0.2	1
	0.2	2	0.4 → 0 + 0.4	0
	0.4	2	0.8 → 0 + 0.8	0
	0.8	2	1.6 → 1 + 0.6	1 → once repetition reached stop.

∴ $(0.1111001)_2$

⇒ 24.6 (decimal) → binary.

Soln

$2 \overline{) 24}$	$2 \overline{) 12}$	$2 \overline{) 6}$	$2 \overline{) 3}$	$2 \overline{) 1}$
$\frac{24}{0}$	$\frac{12}{0}$	$\frac{6}{0}$	$\frac{2}{1}$	$\frac{1}{1}$

$0.6 \times 2 = 1.2 = 1 + 0.2 = \underline{1}$

$0.2 \times 2 = 0.4 = 0 + 0.4 = \underline{0}$

$0.4 \times 2 = 0.8 = 0 + 0.8 = \underline{0}$

$0.8 \times 2 = 1.6 = 1 + 0.6 = \underline{1}$

$0.6 \times 2 = 1.2 = 1 + 0.2 = \underline{1}$

∴ Ans ⇒ $(11000.10011)_2$

⇒ Find 1's complement of $(1101)_2 \Rightarrow \underline{\underline{0010}}$ (Ans)

⇒ Find 1's complement of $(10111001)_2 \Rightarrow \underline{\underline{01000110}}$ (Ans)

⇒ Find 2's complement of $(1001)_2 \Rightarrow$

Soln

1 0 0 1	
0 1 1 0	→ 1's
+	1
0 1 1 1	→ 2's complement.

⇒ Find 2's complement of $(10100011)_2$

Solⁿ $01011100 \rightarrow 1's$

$$\begin{array}{r} 1 \\ + \\ 01011100 \\ \hline 10101101 \end{array} \rightarrow 2's$$

⇒ Subtract $(101011)_2$ from $(111001)_2$ using 1's complement method

Solⁿ

$$\begin{array}{r} 111001 \\ - 010100 \\ \hline 101101 \end{array} \rightarrow 1's \text{ of } (101011)_2$$

⇒ Trick to find 2's complement directly.

Solⁿ (1001) 1 → write the same values till we encounter 1st one (1)
2 → then after that change the values from right

$$\begin{array}{r} 1001 \\ \downarrow \\ 0111 \text{ (Ans)} \end{array}$$

ii) $10100011 \rightarrow 01011101 \text{ (Ans)}.$

⇒ Addition of binary :

i) $110101 + 011010$

$$\begin{array}{r} 11 \\ 110101 \\ + 011010 \\ \hline 1001111 \end{array}$$

we must carry 1 if we get 1+1

Rules for addition

A	B	Sum	Carry
0 + 0		0	0
0 + 1		1	0
1 + 0		1	0
1 + 1		0	1

⇒ Subtraction of binary :

i) when we get carry.

$(110101) - (100101)$

↓ 1's

$110101 + 011010$

$$\begin{array}{r} 11 \\ 110101 \\ + 011010 \\ \hline 1001111 \end{array}$$

where carry 1

$$\begin{array}{r} 1 \\ 1001111 \\ + 1 \\ \hline 1010000 \text{ (Ans)} \end{array}$$

ii) when we don't get carry.

$101011 - 111001$

↓ 1's

$101011 + 000110$

$$\begin{array}{r} 11 \\ 101011 \\ + 000110 \\ \hline 110001 \end{array}$$

↓ 1's

$$001110 \text{ (Ans)}$$

Rules for subtraction in binary.

A	B	diff. sum	carry
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

laws of Boolean Algebra.

i) Commutative $\Rightarrow A+B = B+A$
 ii) Associative $\Rightarrow AB = BA$
 iii) Distributive $\Rightarrow A(B+C) = (A+B)(A+C)$
 $(AB)C = A(BC)$

$$A(B+C) = AB + AC$$

Addition rules in Boolean Algebra :

$$* A + AB = A$$

$$* A(A+B) = A$$

$$* A + \bar{A}B = A+B$$

$$* (A+B)(A+C) = A+BC$$

$$A + \bar{A}B = A+B$$

$$\begin{aligned}
 A + \bar{A}B &= A + AB + \bar{A}B \\
 &= A + B(A + \bar{A}) \\
 &= A + B
 \end{aligned}$$

$$A + AB = A$$

$$\Rightarrow A(1+B) \Rightarrow A(1) = A$$

$$A(A+B) = AA + AB$$

$$= A + A - A$$

$$= A$$

$$(A+B)(A+C) = AA + AC + BA + BC$$

$$= A(\bar{A}+B) + C(\bar{A}+B)$$

$$= (A+B)(A+C)$$

$$= A + AC + BA + BC \quad (\because AA=A)$$

$$= A(1+B+C) + BC$$

$$= A(1+D) + BC$$

$$= A(1) + BC = A+BC$$

Theorem's in Boolean Algebra :

$$\rightarrow \text{De Morgan's Theorem : } (\overline{AB} = \bar{A} + \bar{B}) \quad (\overline{A+B} = \bar{A}\bar{B})$$

$$\rightarrow \text{Consensus Theorem : } (AB + \bar{A}C + BC = AB + \bar{A}C)$$

LAWS OF Boolean Algebra :

And

OR

*

~~$(A+B)(\bar{A}+\bar{B})$~~

$$A + (\bar{A} \cdot B) = \bar{A} \cdot \bar{B} + A + B$$

$$A \cdot 0 = 0$$

$$A + 0 = A$$

$$A \cdot A = A$$

$$A + A = A$$

$$A \cdot 1 = A$$

$$A + 1 = 1$$

$$A \bar{A} = 0$$

$$A + \bar{A} = 1$$

⇒ Solve using Consensus Theorem, $\overline{AB} + AC + \overline{BC} + \overline{BC} + AB$

Soln

$$\frac{\overline{AB} + AB + AC + \overline{BC} + \overline{BC}}{1 + AC + \overline{BC} + \overline{BC}}$$

⇒ Reduce expression

$$\overline{AB} + \overline{A} + AB$$

Soln

$$\begin{array}{l} \overline{A} + \overline{B} + \overline{A} + AB \\ \overline{A} + \overline{B} + AB \\ \overline{A} + \overline{B} + A \\ 1 + \overline{B} \end{array}$$

$$\overline{AB} + \overline{A} + AB$$

$$1 + \overline{A} = 1 = 0$$

$$(\because \overline{AB} + AB = 1)$$

$$1 - B + AB$$

$$1 - B(1 - A)$$

$$1 + \overline{B} = 1 = 0 \text{ (Ans.)}$$

OR, AND, NOT Gates using Universal gates (NAND, NOR)

i) NOT :



using NAND.

ii) AND :



using 2 NANDS.

iii) OR :




using 3 NANDS.

i) NOT :



using NOR

ii) AND :

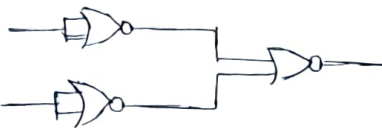

using 3 NOR.

iii) OR :



using 2 NOR.

⇒ using demorgan find $A + B(\overline{C + DE})$

Soln

$$A + B(\overline{C + DE})$$

$$\underline{A + B\overline{C}DE}$$

(or)

$$A + B(\overline{C + \overline{D + E}})$$

$$A + B(\overline{C} \cdot D \cdot E)$$

$$\underline{A + B\overline{C}DE}$$

BINARY \longrightarrow OCTA :

$\Rightarrow (0110100)_2 \longrightarrow (\quad)_8$

Solⁿ

means
(000) $\begin{array}{ccc} \nearrow & & \\ 0 & 110 & 100 \\ \downarrow & \downarrow & \downarrow \\ 0 & 6 & 4 \end{array}$

$\therefore \underline{\underline{(064)_8}}$

$\Rightarrow (1110110)_2$

Solⁿ

$\begin{array}{ccc} 001 & 110 & 110 \\ \downarrow & \downarrow & \downarrow \\ 1 & 6 & 6 \end{array}$

$\therefore \underline{\underline{(166)_8}}$

Decimal to hexadecimal

$\Rightarrow (14)_{10}$

Solⁿ $\begin{array}{r} 16 \overline{) 14} \\ \underline{00} \\ 14 \end{array}$

$\therefore \underline{\underline{(E)_{16}}}$ (Ans)

$\Rightarrow (9216)_{10}$

Solⁿ $\begin{array}{r} 16 \overline{) 9216} \\ \underline{16000} \\ 3216 \\ \underline{3200} \\ 16 \end{array}$

$\begin{array}{r|l} 16 & 9216 \\ 16 & 576 - 0 \\ 16 & 36 - 0 \\ 16 & 2 - 4 \\ & 0 - 2 \end{array}$ \swarrow remainders

$\underline{\underline{(2412)_{16}}}$

Hexadecimal to decimal

$\Rightarrow (A2)_{16}$

Solⁿ $\begin{array}{cc} A=10 & 2 \\ \downarrow & \downarrow \\ 16^1 & 16^0 \end{array}$

$(10 \times 16) + (2 \times 1) = \underline{\underline{(162)_{10}}}$

$\Rightarrow (12B7)_{16}$

Solⁿ $\begin{array}{cccc} 1 & 2 & B & 7 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 16^3 & 16^2 & 16^1 & 16^0 \\ \times & \times & \times & \times \\ 1 & 2 & 11 & 7 \end{array}$

$4096 + 512 + 176 + 7$

$= \underline{\underline{(4791)_{10}}}$

decimal $\rightarrow 10$
Octal $\rightarrow 8 \rightarrow 2^3$
binary $\rightarrow 2 \rightarrow 2^1$
~~decimal $\rightarrow 4 \rightarrow 2^2$~~
hexa decimal $\rightarrow 16 \rightarrow 2^4$

000 $\rightarrow 0$
001 $\rightarrow 1$
010 $\rightarrow 2$
011 $\rightarrow 3$
100 $\rightarrow 4$
101 $\rightarrow 5$
110 $\rightarrow 6$
111 $\rightarrow 7$

Hexadecimal

0 $\rightarrow 0$
1 $\rightarrow 1$
2 $\rightarrow 2$
3 $\rightarrow 3$
4 $\rightarrow 4$
5 $\rightarrow 5$
6 $\rightarrow 6$
7 $\rightarrow 7$
8 $\rightarrow 8$
9 $\rightarrow 9$
A $\rightarrow 10$
B $\rightarrow 11$
C $\rightarrow 12$
D $\rightarrow 13$
E $\rightarrow 14$
F $\rightarrow 15$

⇒ Multiply 1011 by 1101

Soln

$$\begin{array}{r}
 1011 \\
 \times 1101 \\
 \hline
 1011 \\
 0000 \\
 1011 \\
 1011 \\
 \hline
 10001111
 \end{array}$$

} Here add of 3 1's occurs

⇒ Divide 11101 by 1100

Soln

$$\begin{array}{r}
 10 \\
 1100 \overline{) 11101} \\
 \underline{1100} \\
 101 \\
 \underline{100} \\
 101
 \end{array}$$

∴ Quotient = $(10)_2 = (2)_{10}$
 Remainder = $(101)_2 = (5)_{10}$

⇒ Divide 110101.110 with 10


Soln

$$\begin{array}{r}
 101010.111 \\
 10 \overline{) 110101.110} \\
 \underline{10} \\
 10 \\
 \underline{10} \\
 1 \\
 \underline{0} \\
 10 \\
 \underline{10} \\
 01 \\
 \underline{0} \\
 11 \\
 \underline{10} \\
 11 \\
 \underline{10} \\
 10 \\
 \underline{10} \\
 0
 \end{array}$$

∴ Quotient → 11010.111
 Rem → 0

⇒ $[(A+B)C]D \rightarrow$ Draw fig.

Soln

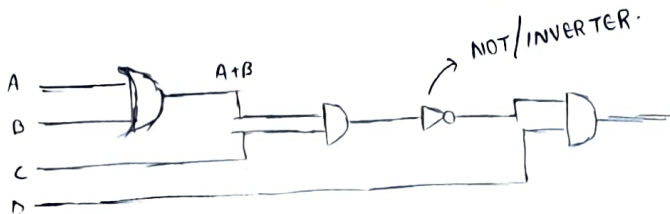

(01)

Boolean Func^N REPRESENTATION

* SOP / s SOP \longrightarrow Standard sum of products

* POS / s POS \longrightarrow Standard product of sum

$$\Rightarrow F(A, B, C) = \bar{A}BC + A\bar{B}C \longrightarrow (SOP)$$

$$\Rightarrow F(A, B, C) = (A+B+C)(\bar{A}+\bar{B}+\bar{C}) \longrightarrow (POS)$$


$$\Rightarrow f(A, B, C, D) = AB\bar{C}\bar{D} + \bar{A}\bar{B}CD + ABC\bar{D} \longrightarrow (SOP)$$

\swarrow convert to POS.

$$\Rightarrow f(A, B, C, D) = (A+B+\bar{C}+\bar{D})(\bar{A}+\bar{B}+C+D)(A+B+C+\bar{D}) \longrightarrow (POS)$$

\Rightarrow Draw ~~diagram~~ digital circuit for $AC + ABC$

Solⁿ

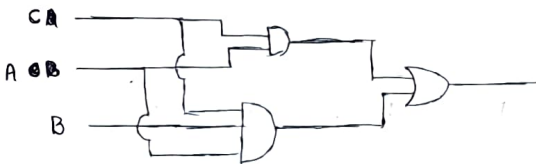

(or)

$$AC(1+B) = AC$$



\longrightarrow SOP [Two input gate]

\Rightarrow Given : $\neg\neg$

Solⁿ

complement \longrightarrow 0

normal \longrightarrow 1.

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1

it is not AND/OR
it is just given in que.

A	B	Y	Product
0	0	0	$\bar{A}\bar{B}$
0	1	0	$\bar{A}B$
1	0	1	$A\bar{B}$
1	1	1	AB

$$\therefore Y = AB + \bar{A}\bar{B} \longleftarrow \text{only take values having } Y=1$$

→ POS (3 2/p gate) :

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Don't

Nosimal → 0

Complement → 1

ABC	Y ₁
000	1
001	1
010	1
011	0
100	1
101	1
110	0
111	1

Take
complement

$$\text{SOP} \rightarrow \therefore Y = ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$\text{POS} \rightarrow Y = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+\bar{C})$$

* Complete Minterm, Maxterm, SOP → SSOP, POS → SPOS, before K-Map.

KARNAUGH MAP [K-Map] : (no. of cells → 2^n cells).

* Two variable K-Map :

$$\hookrightarrow 2^2 = 4$$

A \ B	00	01
0	0	1
1	2	3

* Three variable K-Map : $2^3 = 8$.

A \ BC	00	01	11	10
0	0	1	3	2
1	4	5	7	6

* ~~Two~~ VA

* Four variable K-Map : $2^4 = 16$

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Order to take binary :

$$00 \rightarrow 01 \rightarrow 11 \rightarrow 10$$

Just change one no.

either left or right but not both

To mem. values, convert binary to decimal (or else mem.).

$$\text{ex : } (1111)_2 \rightarrow (15)_{10}$$

$$(1011)_2 \rightarrow (11)_{10}$$

→ Rules for creating group in K-Map :

* No zeros allowed

* Group can be vertical / horizontal but not diagonals.

* Overlapping allowed

* Group should be as large as possible

* Group must contain 2^n cells.

$$\Rightarrow F(A, B) = \sum (0, 2, 3)$$

Soln) $A, B \rightarrow$ Two variable

B \ A	0	1
0	1	0
1	1	1

$\therefore P_1$

A \ B	0	1
0	1	0
1	1	0

P_2

A \ B	0	1
0	1	0
1	1	1

\therefore Put $0 \rightarrow \bar{A}$
 $1 \rightarrow A$

$$\therefore F(A, B) \rightarrow \underline{\underline{B' + A}} \quad (\text{Ans})$$

Step-1 : Draw K-Map according to var

Step-2 : put "1" on cells given in bracket

Step-3 : put binary above box

Step-4 : Take pairs as large as possible

Step-5 : Put values of cell, containing '1'

Step-5 : Cancel values having 0 & 1 both

Step-6 : $\bar{A} \rightarrow 0$
 $A \rightarrow 1$

$$\Rightarrow F(A, B, C) = \sum (0, 1, 2, 3, 5)$$

Soln)

Bc \ A	00	01	11	10
0	1	1	1	1
1	1	0	0	0

P_1

A \ B C	00	01	11	10
0	1	1	1	1
1	1	0	0	0

P_2

A \ B C	00	01	11	10
0	1	1	1	1
1	1	0	0	0

A

$$F(A, B, C) = \underline{\underline{A' + B' + B'C}} \quad (\text{Ans})$$

$$\Rightarrow F(A, B, C, D) = \sum (0, 1, 4, 5, 8, 9, 12, 13)$$

Solⁿ

	CD	00	01	11	10
AB	00	1	1		
	01	1	1		
	11	1	1		
	10	1	1		

	CD	00	01	11	10
AB	00	1	1		
	01	1	1		
	11	1	1		
	10	1	1		

we have to take
group as large as
possible

we can take a
group of 8 or 4 or 2 or 1

∴

E P _i			
A	B	C	D
0	0	0	0
0	0	0	1
0	1	0	0
0	1	0	1
1	1	0	0
1	1	0	1
1	0	0	0
1	0	0	1

∴ C' (Ans).

MINTERM & MAXTERM :

* Minterm → Each individual term in SSOP

* Maxterm → Each individual term in SPOS.

Variable		Minterm	Maxterm
A	B	SSOP	SPOS
0	0	$\bar{A}\bar{B} \rightarrow m_0$	$A+B \rightarrow M_0$
0	1	$\bar{A}B \rightarrow m_1$	$A+\bar{B} \rightarrow M_1$
1	0	$AB \rightarrow m_2$	$\bar{A}+B \rightarrow M_2$
1	1	$AB \rightarrow m_3$	$\bar{A}+\bar{B} \rightarrow M_3$

for ~~minterm~~ ^{SOP} $\begin{cases} 0 \rightarrow \text{complement} \\ 1 \rightarrow \text{normal} \end{cases}$

for POS $\begin{cases} 0 \rightarrow \text{normal} \\ 1 \rightarrow \text{complement} \end{cases}$

* ex : $f(A, B) = AB + \bar{A}B$

Solⁿ it is SOP →

1 1	0 1
AB	$\bar{A}B$
↓	↓
3	1

$$\therefore \underline{\underline{\sum m(1, 3)}}$$

$$\Rightarrow f(A, B) = (A+B) (\bar{A}+B)$$

$$\text{Soln} \quad \begin{matrix} \begin{pmatrix} 0 & 0 \\ A+B \end{pmatrix} & \begin{pmatrix} 1 & 0 \\ \bar{A}+B \end{pmatrix} \\ \downarrow & \downarrow \\ 0 & 2 \end{matrix}$$

$$\therefore \text{SOP} (0, 2)$$

$$\underline{\underline{\pi M (0, 2)}}$$

→ SOP & SSOP :

* SSOP → The function should contain all variables in every product

$$\text{i.e., } AB' + A \quad (\times \text{ SOP}) \quad (\checkmark \text{ SSOP})$$

$$ABC' + A'B \quad (\times \text{ SOP}) \quad (\checkmark \text{ SSOP})$$

$$A'C + AB' + BC \quad (\times \text{ SOP}) \quad (\checkmark \text{ SSOP})$$

* * Converting SSOP to CSOP

$$\Rightarrow AB' + A$$

$$\Rightarrow ABC' + A'B$$

$$\Rightarrow A'C + AB' + BC$$

$$\text{Soln} \quad AB' + A(1)$$

$$\text{Soln} \quad ABC' + A'B(1)$$

$$\text{Soln} \quad A'C(1) + AB'(1) + BC(1)$$

$$AB' + A(B+B')$$

$$ABC' + A'B(C+C')$$

$$A'C(B+B') + AB'(C+C') + BC(A+A')$$

$$AB' + AB + AB'$$

$$ABC' + A'BC + A'BC'$$

$$A'BC + A'CB' + AB'C + AB'C' + BC$$

$$\underline{\underline{AB' + AB}} \quad (\text{SSOP})$$

* → SOP to CSOP :
 → canonical

$$\Rightarrow (A'+B) B$$

$$\Rightarrow (A+B) (B+C') (A'+C)$$

$$\text{Soln} \quad (A'+B) (B+0)$$

$$\text{Soln} \quad (A+B) (B+C'+0) (A'+C+B)$$

$$(A'+B) (B+A \cdot A')$$

$$(A+B+C') (B+C'+AA') (A'+C+BB')$$

$$(A'+B) (B+A) (B+A')$$

$$(A+B+C) (A+B+C') (B+C'+A) (B+C'+A') (A'+C+B)$$

$$(A'+C+B')$$

$$\Rightarrow \underline{\underline{(A'+B) (A+B)}}$$

$$\underline{\underline{(A+B+C) (A+B+C') (B+C'+A) (A'+C+B) (A'+C+B')}}$$

⇒ Draw K-Map for

$$f = A'B'C'D + ABC'D + A'BCD + ABCD + A'B'C'D'$$

Soln

AB \ CD	00	01	11	10
00	1			
01		1	1	
11		1	1	
10				

P

A	B	C	D
0	1	0	1
0	1	1	1
1	1	1	1
1	1	0	1

Q

$$\therefore f = \underline{\underline{A'B'C'D' + BD}} \quad (\text{Ans})$$

→ K-Map for POS :

$$\Rightarrow f = (A'+B)(A+B)$$

Soln

A \ B	0	1
0	0	0
1	0	1

A

A	B
0	0
0	1
1	0
1	1

$$\underline{\underline{B}} \quad (\text{Ans})$$

$$\Rightarrow F = (A+B+\bar{C})(A+B'+C')(A+B+C)$$

Soln

AB \ BC	00	01	11	10
00	0	0	0	
01				
11				
10				

P₁

A	B	C
0	0	0
0	0	1
1	0	0
1	0	1

A+B

P₂

A	B	C
0	0	1
0	1	1
1	1	1
1	0	1

A'C'

$$\therefore \underline{\underline{F = (A+B)(A+C')}} \quad (\text{Ans})$$

$$\Rightarrow F = \Pi(6, 7, 15)$$

Soln

AB \ CD	00	01	11	10
00	1			
01			0	0
11			0	
10				

P₁

A	B	C	D
0	1	1	1
0	1	1	0
1	1	1	1
1	1	1	0

A+B'+C'

P₂

A	B	C	D
0	1	1	1
0	1	1	0
1	1	1	1
1	1	1	0

B'+C'+D'

$$\therefore \underline{\underline{F = (A+B'+C')(B'+C'+D')}} \quad (\text{Ans})$$

Kmap with don't care condition.

$$\Rightarrow f(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 12, 13, 14) + \underbrace{\sum d(1, 4, 11, 15)}_{\text{don't care}}$$

Soln

CD \ AB	00	01	11	10
00	1	x	1	1
01	x		1	1
11	1	1	x	1
10			x	

x \rightarrow can be 1 or 0 depending on pairing range.

only include 1 'x' in grp.

$\therefore P_1$

A	B	C	D
0	0	1	1
0	0	1	0
0		1	1
0	1	1	0

$\bar{A}C$

P_2

A	B	C	D
0	0	1	1
0	0	0	1
0	0	1	1
0	0	1	0

$\bar{A}\bar{B}$

P_3

A	B	C	D
1	1	0	1
1	1	0	1
1	1	1	1
1	1	1	0

AB

$$\therefore F = \underline{\underline{A'B' + A'C + AB}}$$

$$\Rightarrow f(A, B, C, D) = \pi M(5, 8, 9, 10) \pi D(1, 4, 11, 15)$$

Soln

CD \ AB	00	01	11	10
00		x		
01	x	0		
11			x	
10	0	0	x	0

P_1

A	B	C	D
0	1	0	0
0	1	0	1

$AB'C$

P_2

A	B	C	D
0	0	0	1
0	0	0	1

ACD'

P_3


A	B	C	D
1	0	0	0
1	0	0	1
1	0	1	1
1	0	1	0

$A'B$

$$\therefore \underline{\underline{(A+B'+C)(A+C+D')(A'+B)}}$$

CORNERING IN K-Map :
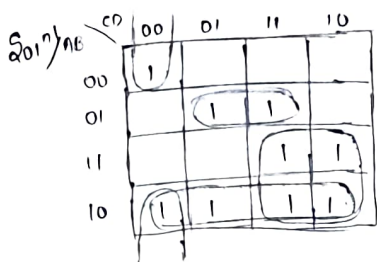
$$\Rightarrow f(A, B, C, D) = \sum (0, 5, 7, 8, 9, 10, 11, 14, 15)$$



$$P_1$$

A	B	C	D
0	0	0	0
1	0	0	0

$$B'C'D'$$

$$P_2$$

A	B	C	D
0	1	0	1
0	1	1	1

$$A'BD$$

$$P_3$$

A	B	C	D
1	1	1	1
1	1	1	0
1	0	1	1
1	0	1	0

$$AC$$

$$P_4$$


A	B	C	D
1	0	0	0
1	0	0	1
1	0	1	1
1	0	1	0

$$AB'$$

$$\therefore B'C'D' + A'BD + AC + AB' = f$$

Always verify K-Map : (To get marks draw fig.) ^{imp} do in every K-map que.

A B C D

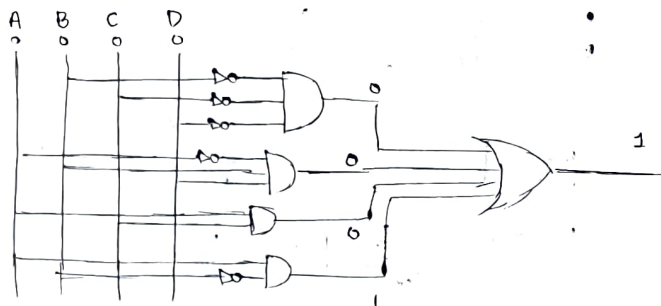

Verified

* Mux & De-bux ~~can~~ will come in FAT.


HALF ADDER :



A	B	Sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\therefore S = A'B + AB' = A \oplus B$$

$$C = AB$$

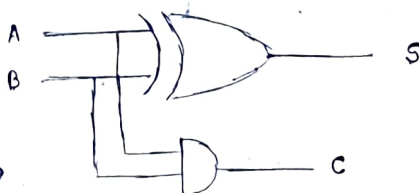


$$\text{ex: } \begin{array}{r} 1 \\ 01 \\ + 11 \\ \hline 0 \end{array}$$

$$\therefore \text{carry} = 1$$

$$\text{Sum} = 0$$

in half adder
we cannot add
carry :-


K-Map (Sum)

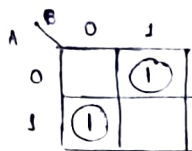

$$Y = \bar{A}B + A\bar{B}$$

$$Y = \underline{\underline{A \oplus B}}$$

K-Map (Carry)


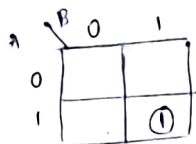


$$Y = \underline{\underline{AB}}$$

Full Adder:



A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

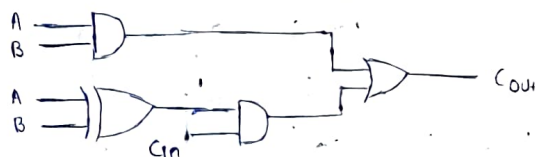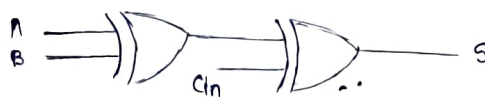


$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$C_{out} = \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + BC_{in})$$

$$= \bar{A}(B \oplus C_{in}) + A(\overline{B \oplus C_{in}})$$


$$= \bar{A}X + A\bar{X}$$
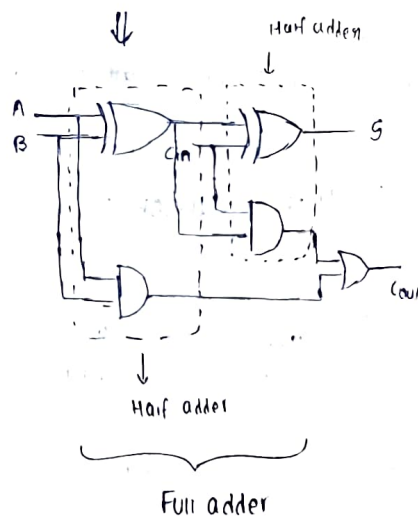
$$= \underline{\underline{A \oplus X}} = \underline{\underline{A \oplus B \oplus C_{in}}}$$




$$C_{out} = \bar{A}BC_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC$$

Red

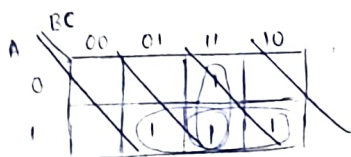

$$C_{out} = A$$
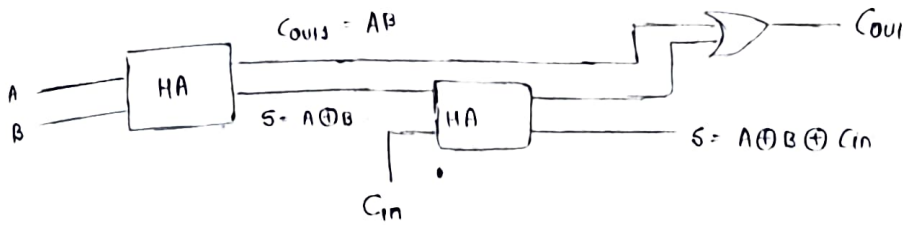
$$C_{out} = AB(\bar{C}_{in} + C_{in}) + C_{in}(\bar{A}B + A\bar{B}) = AB + C_{in}(A \oplus B)$$



} Full adder
using half
adders

KMap for sum :

BC	00	01	11	10
A				
0		1		1
1	1		1	

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$S = A \oplus B \oplus C \quad \text{solve:}$$

K-Map for carry :

BC	00	01	11	10
A				
0			1	
1		1	1	1


	P ₁	P ₂	P ₃
	A B C	A B C	A B C
	1 0 1	0 1 1	1 1 1
	1 1 1	1 1 1	1 1 0
	AC	BC	AB

$$\therefore C = AC + BC + AB$$

$$\therefore C_{out} = AC + BC + AB = AB + C_{in}(A \oplus B)$$

$$S = A \oplus B \oplus C$$

HALF SUBTRACTOR :

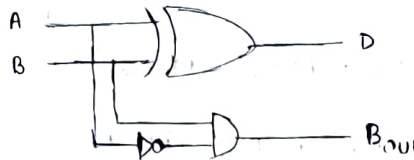

A	B	D	B _{out}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\begin{array}{r} 10 \\ - 01 \\ \hline 1 \end{array}$$

$$\therefore D = 1$$

$$B_{out} = 1$$

$$D = \bar{A}B + A\bar{B} = A \oplus B$$

$$B = \bar{A}B$$

K-Map (sum)

BC	0	1
A		
0		1
1	1	

$$S = \bar{A}B + A\bar{B}$$


K-Map (Borrow)

BC	0	1
A		
0		1
1		



$$B_{out} = \bar{A}B$$

in half subtractor
we cannot subtract
borrow.


FULL SUBTRACTOR :

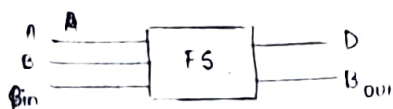

A	B	B_{in}	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

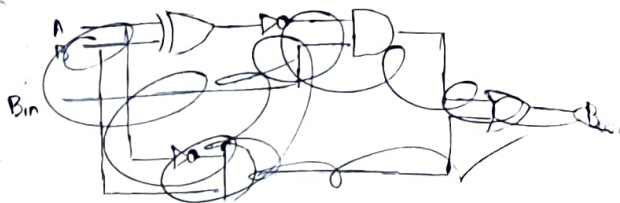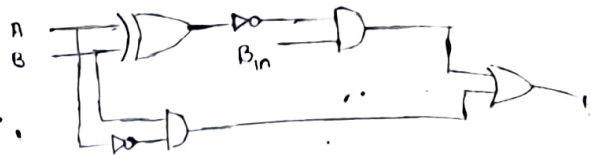

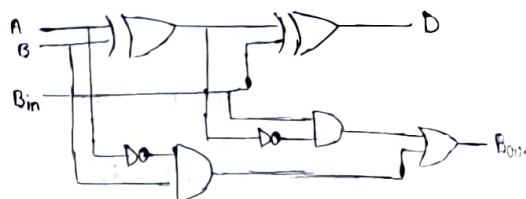
$$\begin{aligned}
 D &= \bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + A\bar{B}\bar{B}_{in} + AB B_{in} \\
 &= \bar{B}_{in} (\bar{A}B + A\bar{B}) + B_{in} (\bar{A}\bar{B} + AB) \\
 &= \bar{B}_{in} (A \oplus B) + B_{in} (\overline{A \oplus B}) \\
 &= \bar{B}_{in} X + B_{in} \bar{X} \\
 &= B_{in} \oplus X \\
 &= B_{in} \oplus A \oplus B
 \end{aligned}$$



Full Subtractor
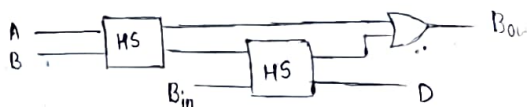
$$\begin{aligned}
 B_{out} &= \bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + \bar{A}B B_{in} + AB B_{in} \\
 &= \bar{A}B (\bar{B}_{in} + B_{in}) + AB_{in} (\bar{A}\bar{B} + AB) \\
 &= \bar{A}B + B_{in} (\overline{A \oplus B})
 \end{aligned}$$




Mux AND Demux



Multiple input
to
single output

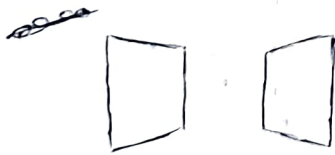~~multiple~~ or
single input
to
multiple output



Mux

De-Mux

(Many to one)

(One to many)


$$\text{Mux} \longrightarrow 2^n - 1$$

$$\text{De-Mux} \longrightarrow 1 - 2^n$$

$$2^n - n \longrightarrow \text{Encoding}$$

$$n - 2^n \longrightarrow \text{Decoding}$$

→ 4x1 Mux :

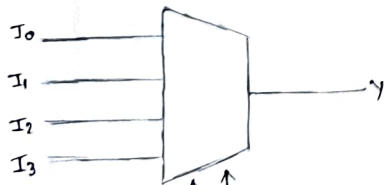

S_1, S_0 ← in this order only.


4 inputs,

$$\text{so, } 2^n = 4$$


$$n = 2 \longrightarrow \text{i.e., } S_0, S_1$$

\bar{S}_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
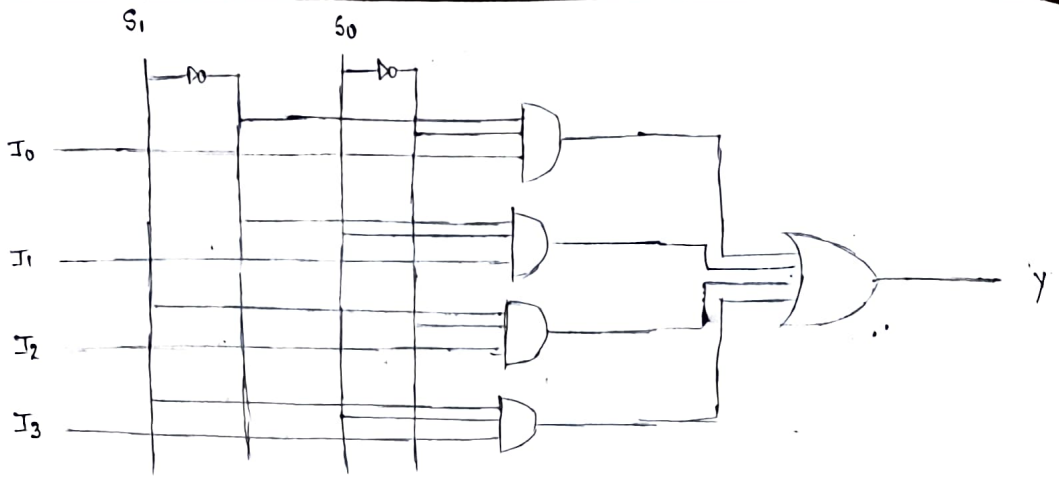
$$\therefore Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



→ De-Mux: (1x4)

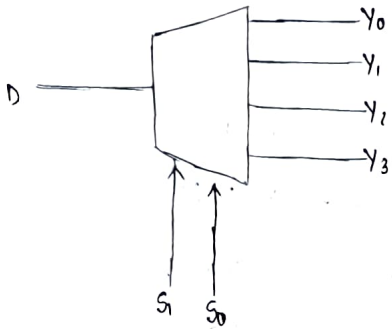


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	D
0	1	0	0	D	0
1	0	0	D	0	0
1	1	D	0	0	0

$$Y_0 = \bar{S}_1 \bar{S}_0 D$$

$$Y_1 = \bar{S}_1 S_0 D$$

$$Y_2 = S_1 \bar{S}_0 D$$

$$Y_3 = S_1 S_0 D$$

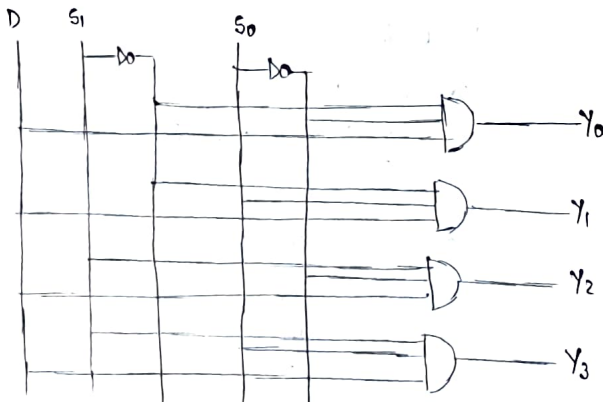


* SOP = $\overline{\text{POS}}$

* POS = $\overline{\text{SOP}}$

← In interchange eqⁿ

SOP ↔ POS

→ Mux : (8x1)

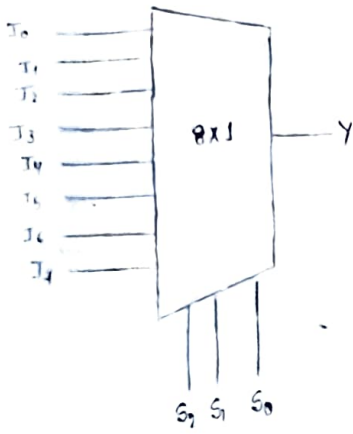


S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Draw diag.

$$\underline{2^3 = 8}$$

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \dots + S_2 S_1 S_0 I_7$$

→ De Mux : (1x8)

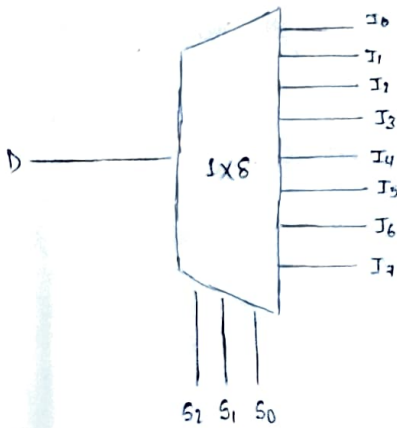

S_2	S_1	S_0	I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0
0	0	0	0	0	0	0	0	0	0	D
0	0	1	0	0	0	0	0	0	D	0
0	1	0	0	0	0	0	0	D	0	0
0	1	1	0	0	0	0	D	0	0	0
1	0	0	0	0	0	D	0	0	0	0
1	0	1	0	0	D	0	0	0	0	0
1	1	0	0	D	0	0	0	0	0	0
1	1	1	D	0	0	0	0	0	0	0

$$I_0 = \bar{S}_2 \bar{S}_1 \bar{S}_0 D \quad \dots \quad I_6 = S_2 S_1 \bar{S}_0 D$$

$$I_7 = S_2 S_1 S_0 D$$

Draw diag:

* design full wave and half wave rectifiers .